

Analog IC Design – Xschem/Ngspice and ADT

Lab 01

LPF Simulation and MOSFET Characteristics

Intended Learning Objectives

This lab is divided into two parts:

- In Part 1 you will
 - Get familiar with Xschem/Ngspice, and ADT IC design tools.
 - Learn the different types of simulations (transient, ac).
 - Learn how to run parametric sweeps.
- In Part 2 you will
 - Compare the behavior of PMOS and NMOS transistors.
 - Compare the behavior of short-channel and long-channel MOSFETs.


PART 1: Low Pass Filter Simulation (LPF)

1. Transient Analysis

- 1) Design a first order low pass filter that has $R = 1k\Omega$ and 1ns time constant.
- 2) Apply a square wave input with $T_{high} = Pulse\ Width = 10ns$, $T_{clk} = Period = 20ns$, and $T_{rise} = T_{fall} = 100ps$.
- 3) Report transient analysis results for two periods.
- 4) Calculate rise and fall time (10% to 90%).
- 5) Compare simulation with analytical results in a table.
- 6) Do parametric sweep for $R = 1: 1: 5k\Omega$. Report overlaid results. Comment on the results.

Solution Steps:

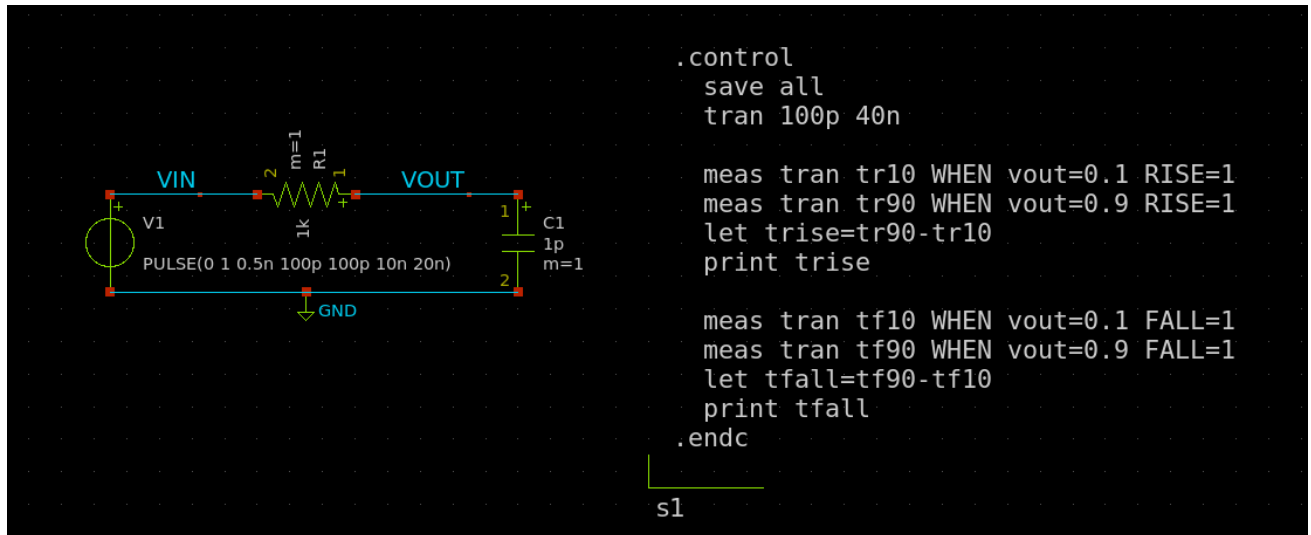- 1) Create a new work directory.
- 2) Create the schematic of the low pass filter as shown below
 - Use shift+I to insert symbols
 - Use search bar to search for “res” (resistor), “capa” (Capacitor), and vsource (Voltage Source).
 - Use “Shift+R” to rotate symbols
 - To edit the properties of a symbol: select the symbol then press ‘Q’
 - Use “Alt+L” to label the wires
 - To create a pulse, change the “vsource” value to “PULSE(0 1 0.5n 100p 10n 20n)”, refer to section 4.1.1 in ngspice manual for more details.



3) Run Simulations

- Press “Simulation”, then “configure simulators and tools”, make sure “ngspice batch” is selected.
- Insert “code_shown”, change its value to the following code:

```
.control
save all
tran 100p 40n

meas tran tr10 WHEN vout=0.1 RISE=1
meas tran tr90 WHEN vout=0.9 RISE=1
let trise=tr90-tr10
print trise

meas tran tf10 WHEN vout=0.1 FALL=1
meas tran tf90 WHEN vout=0.9 FALL=1
let tfall=tf90-tf10
print tfall
.endc
```

- Press “netlist” on the top right.
- Press “Simulate”.

4) Plot Results

- Press “Simulation” then “Add waveform graph”.
- Press “Simulation” again then “Add waveform reload launcher”.
- Press “ctrl” and “the green left arrow” to load the results.
- Double click on the waveform, choose the outputs to plot, then press add.

Calculate rise and fall time (10% to 90%).

- change simulator to interactive
- Using “meas” Command (included in the previous code)

Use the following code for parametric sweep:


```
.control
save all
let Rstart=1k
let Rstop=5k
let Rstep=1k
let Ract=1k
while Ract le Rstop
  alter R1 Ract
  tran 100p 40n
  meas tran tr10 WHEN vout=0.1 RISE=1
  meas tran tr90 WHEN vout=0.9 RISE=1
  let trise=tr90-tr10
  print trise
  let Ract=Ract+Rstep
  reset
  set appendwrite
  write RC_CKT.raw
end
plot tran1.v(vout) tran2.v(vout) tran3.v(vout)
tran4.v(vout) tran5.v(vout)
.endc
```

2. AC Analysis

- 1) Report Bode Plot (magnitude and phase) for the previous LPF.
- 2) Calculate DC gain and 3dB bandwidth.
- 3) Compare simulation with analytical results in a table.
- 4) Do parametric sweep for $R = 1, 10, 100, 1000k\Omega$. Report overlaid results. Comment on the results.

Solution Steps:

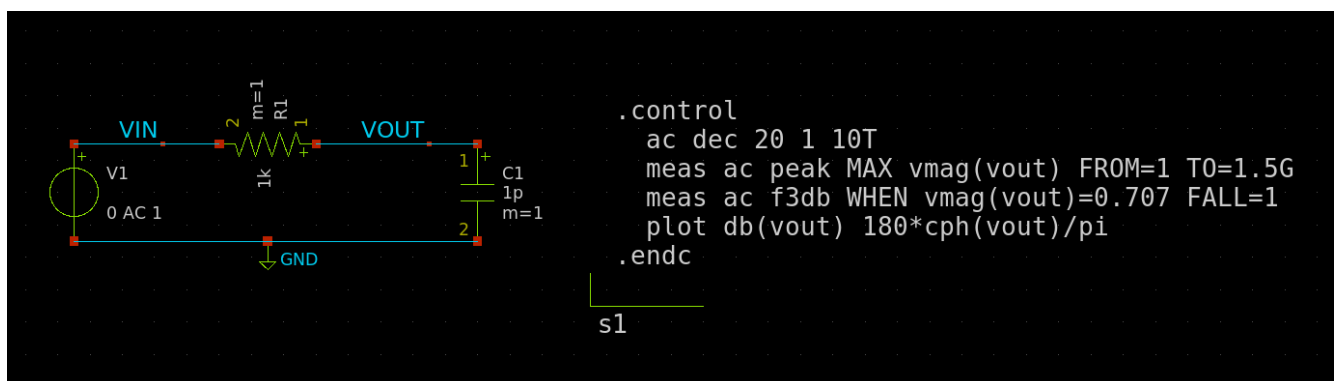- 1) Change the Vsource value to "0 AC 1"
- 2) Change the simulator to be interactive
- 3) Netlist + Simulate
- 4) Calculate DC gain and 3 dB bandwidth using the code shown in schematic, results can be found in terminal.



- 5) Use "plot db(vout) 180*cph(vout)/pi" in the command to report the bodeplot.

```
.control
save all
ac dec 20 1 10T
meas ac peak MAX vmag(vout) FROM=1 TO=1.5G
meas ac f3db WHEN vmag(vout)=0.707 FALL=1
plot db(vout) 180*cph(vout)/pi
.endc
```

6) Use the following code to perform parametric sweep:

```
.control
save all
let Rstart=1k
let Rstop=1000k
let Rstep=10
let Ract=1k

while Ract le Rstop
alter R1 Ract
ac dec 20 1 10T
meas ac peak MAX vmag(vout) FROM=1 TO=1.5G
meas ac f3db WHEN vmag(vout)=0.707 FALL=1
let Ract=Ract*Rstep
reset
set appendwrite
write RC_CKT.raw
end

let BP1=ac1.v(vout)
let BP2=ac2.v(vout)
let BP3=ac3.v(vout)
let BP4=ac4.v(vout)

plot db(BP1) db(BP2) db(BP3) db(BP4)
.endc
```

Part 2: MOSFET Characteristics

1. I_D vs V_{GS}

- 1) Plot $I_D - V_{GS}$ characteristics for NMOS and PMOS devices. Set $V_{DS} = V_{DD}$, and $V_{GS} = 0:10m:V_{DD}$. Use $V_{DD} = 1.2V$ for 130nm technology and $V_{DD} = 1.8V$ for 180nm technology. Plot the results overlaid for the following:
 - Short channel device: $W = 1\mu m$ and $L = 200nm$
 - Long channel device: $W = 10\mu m$ and $L = 2\mu m$. Hint: Set L as a parameter and set $W = 5 \times L$
- 2) Comment on the differences between short channel and long channel results.
 - Which one has higher current? Why?
 - Is the relation linear or quadratic? Why?
- 3) Comment on the differences between NMOS and PMOS.
 - Which one has higher current? Why?
 - What is the ratio between NMOS and PMOS currents at $V_{GS} = V_{DD}$?
 - Which one is more affected by short channel effects?

2. g_m vs V_{GS}

- 1) Plot g_m vs V_{GS} for NMOS device. Set $V_{DS} = V_{DD}$, and $V_{GS} = 0:10m:V_{DD}$. Plot the results overlaid for the following:
 - Short channel device: $W = 1\mu m$ and $L = 200nm$
 - Long channel device: $W = 10\mu m$ and $L = 2\mu m$.
- 2) Comment on the differences between short channel and long channel results.
 - Does g_m increase linearly? Why?
 - Does g_m saturate? Why?


3. I_D vs V_{DS}

- 1) Plot $I_D - V_{DS}$ characteristics for NMOS device. Set $V_{GS} = 0:10m:V_{DD}$, and $V_{DS} = 0:0.2:V_{DD}$ (nested sweep). Plot the results overlaid for the following:
 - Short channel device: $W = 1\mu m$ and $L = 200nm$
 - Long channel device: $W = 10\mu m$ and $L = 2\mu m$.
- 2) Comment on the differences between short channel and long channel results.
 - Which one has higher current? Why?
 - Which one has higher slope in the saturation region? Why?

Solution Steps:

- 1) Open terminal in "home/tare/ADT_Working_Directory" folder
- 2) Type `./start_adt.sh` in the terminal to start ADT.
- 3) Load Luts from "home/tare/LUTs".
- 4) Open "Sizing Assistant" tap.
- 5) Edit "LUT settings" according to the required as shown on the right of the figure below.
- 6) Plot using the "Results" section choose appended if needed as shown in the figure.

ID vs VGS

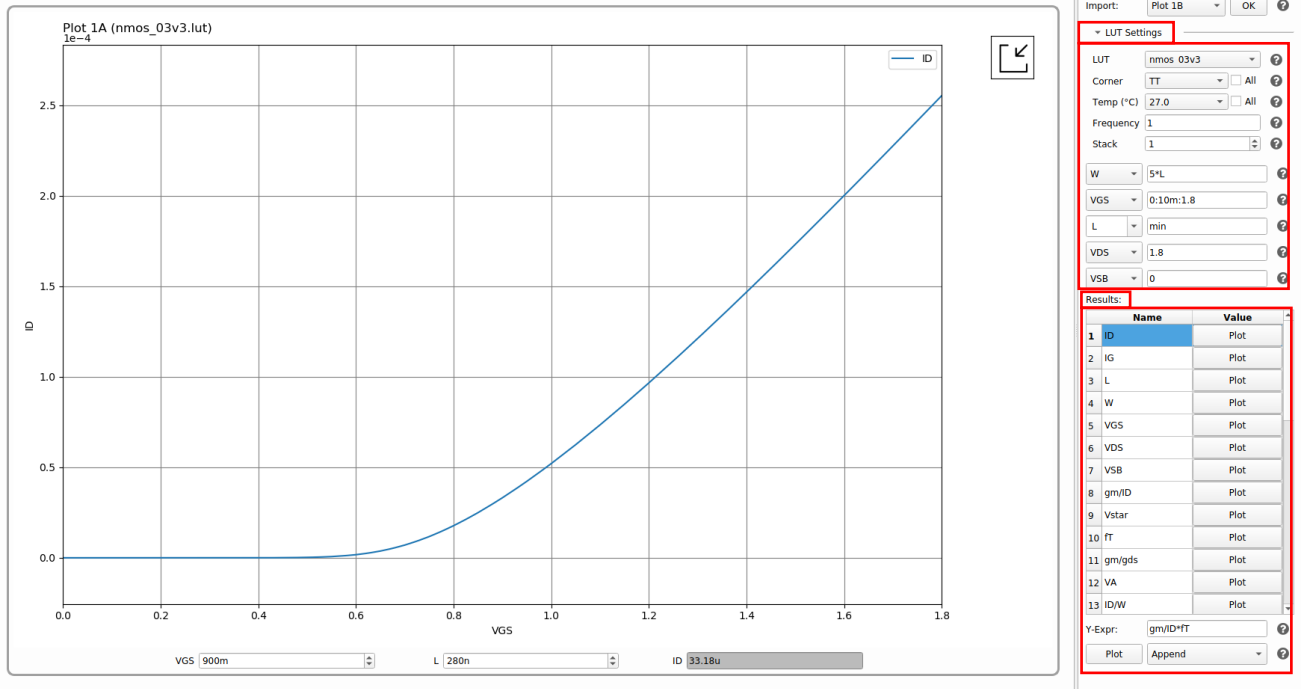

Lab Summary

- In Part 1 you learned
 - How to run transient simulations.
 - How to run ac-analysis simulations.
 - How to run parametric sweeps.
- In Part 2 you learned
 - How to plot the transistors I/V characteristics using DC analysis.
 - How to plot the transistors I/V characteristics using parametric sweeps.
 - The difference in transistor characteristics between an NMOS and a PMOS transistor.
 - The difference in transistor characteristics between a short-channel and a long-channel MOSFET.
 - How the g_m of the transistor behaves vs V_{GS} .