

Analog IC Design – Xschem and Master Micro Tools**Lab 06****Differential Amplifier****Intended Learning Objectives**

In this lab you will:

- Design a differential amplifier circuit using the Sizing Assistant (SA).
- Learn how to simulate the small-signal differential characteristics of a differential amplifier.
- Learn how to simulate the small-signal common-mode characteristics of a differential amplifier.
- Learn how to simulate the large-signal differential characteristics of a differential amplifier.
- Learn how to simulate the large-signal common-mode characteristics of a differential amplifier.

Part 1: Differential Amplifier Design

- 1) We want to design a resistive loaded differential amplifier with the specifications below.


NOTE: that the bias current is split between two transistors; each transistor gets $I_D = 20\mu A$.

Parameter	
Supply (V_{DD})	1.8V
Bias current (I_{SS})	40 μA
Differential gain	8
CM output level ¹	$V_{DD}/3$
Load capacitance	1pF

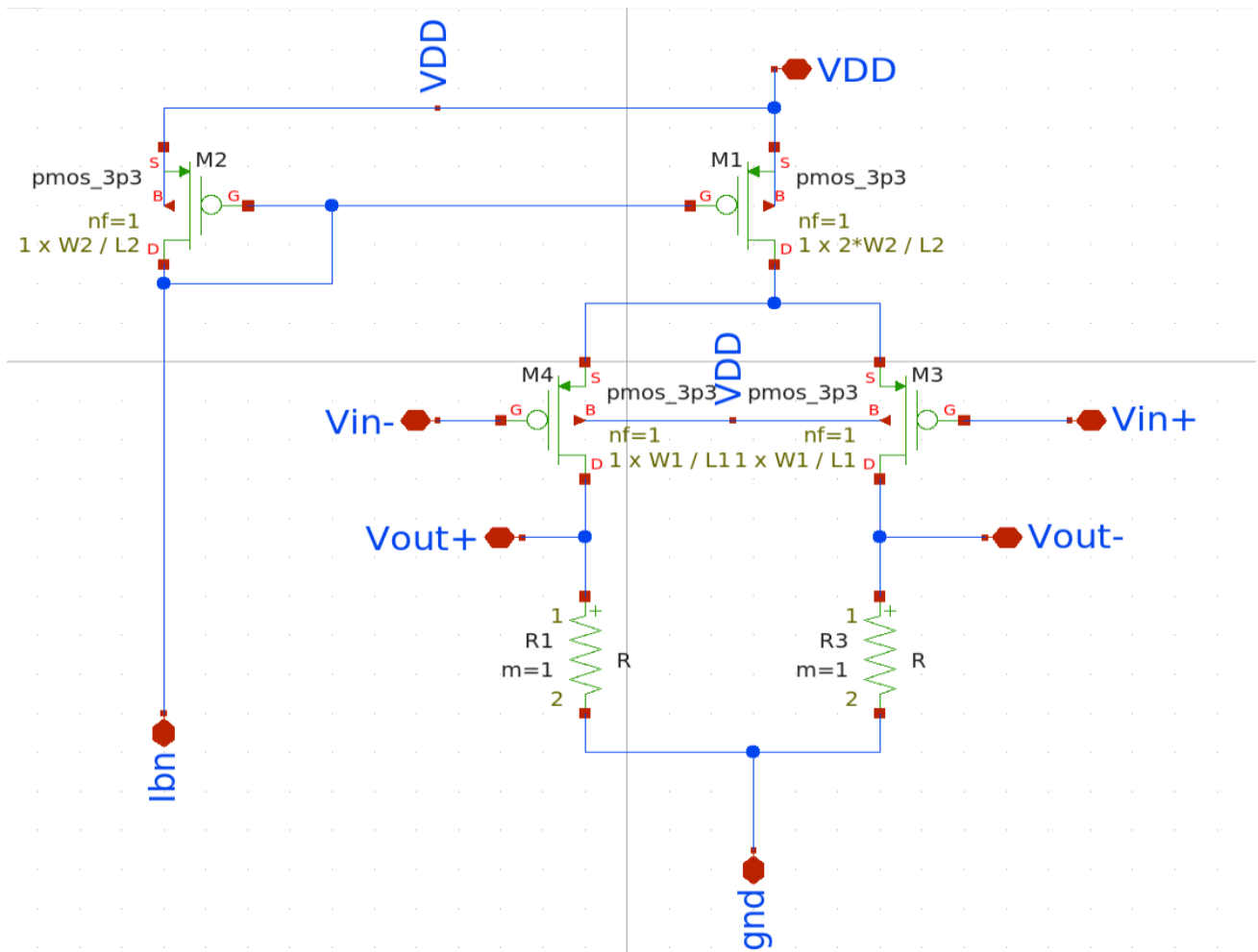- 2) Since the required output level is closer to the ground rail, we will use a PMOS input stage. Assume the PMOS will not be placed in a dedicated well to save the area -Body cannot be connected to floating source-. Assume we will use a simple current mirror for biasing. The design schematic is shown below.

➔ Xschem Hint: You can add labels (names) to nets (wires) using the hotkey "Alt+l" and create ports using the hotkey "shift + l → devices → iopin".

¹ The supply voltage is divided between the tail current source, the input stage, and the resistive load. The tail current source needs a good voltage drop (V_{DS}) for higher output resistance and good CMRR. The input stage needs a good voltage drop (V_{DS}) for higher output resistance and to allow good signal swing. The resistive load needs a good voltage drop to allow a good swing and to give higher gain. Note that $I_{SS}R_D = 2V_{out-CM}$ must be smaller than $(V_{DD} - V_{dsat-tail})$ for proper large signal characteristics (why?).



3) Choose R_D to meet the CM output level spec.

4) The differential amplifier gain is given by

$$|A_v| \approx g_m(R_D || r_o)$$

5) We will choose L to set $r_o \gg R_D \rightarrow r_o = 10 \times R_D$

$$|A_v| \approx 0.91 \times g_m R_D = 0.91 \times \frac{2I_D}{V^*} \times R_D = \frac{1.82V_{R_D}}{V^*}$$

6) Choose V^* to meet the differential gain spec.

$$V^* = \frac{1.82V_{R_D}}{|A_v|}$$

7) Assume we will set V_{DS} of the tail current source to 300mV to allow more output swing. **Report the input pair sizing using SA.**

ID	20u	?
Vstar	136m	?
ro	30*10k	?
VDS	0.9	?
VSB	0.3	?

- 8) Given the above assumption for V_{DS} of the tail current source, **calculate** the required CM input level.
- 9) The tail current source has the following specifications:

Parameter	
Input current	$20\mu A$
Percent mismatch: $\sigma(I_{out})/I_{out}$	$\leq 2\%$
Compliance voltage	$\leq 200mV$
Area	Minimize

- 10) Use SA to plot the sizing at a constant $\sigma(I_{out})/I_{out}$.

$$\frac{\sigma(I_{out})}{I_{out}} = \frac{\sqrt{1 + \frac{1}{m}} \times \frac{A_{VT}}{\sqrt{WL}} \times mg_m}{mI_D} \times 100$$

Where m is the mirroring ratio, $A_{VT} = 5mV \cdot \mu m$ is Pelgrom's coefficient, and the $\sqrt{1 + \frac{1}{m}}$ factor is due to taking the difference between two random variables (V_{TH} of the two current mirror transistors).

From VM were open ADT

1. Open a terminal in the directory: "/home/tare/ADT_Working_Directory"

2. Run the command: "./start_adt.sh"


- Load LUTs files (file - load LUT - open nmos_3p3).
- Open Sizing Assistant and set the parameters as shown below.
- to plot the sizing at a constant σ

$\text{sqrt}(1.5) * 5 * 1E-3 / \text{sqrt}(W * L * 1E12) * gm / ID * 100$

The screenshot shows the 'LUT settings' window in the ADT Sizing Assistant. The parameters are set as follows:

- LUT: pmos_03v3
- Corner: TT
- Temp (°C): 27.0
- Frequency: 1
- Stack: 1
- ID: 20u
- Vstar: 100m:1m:200m
- /ID*100: 2
- VDS: 0.3
- VSB: 0

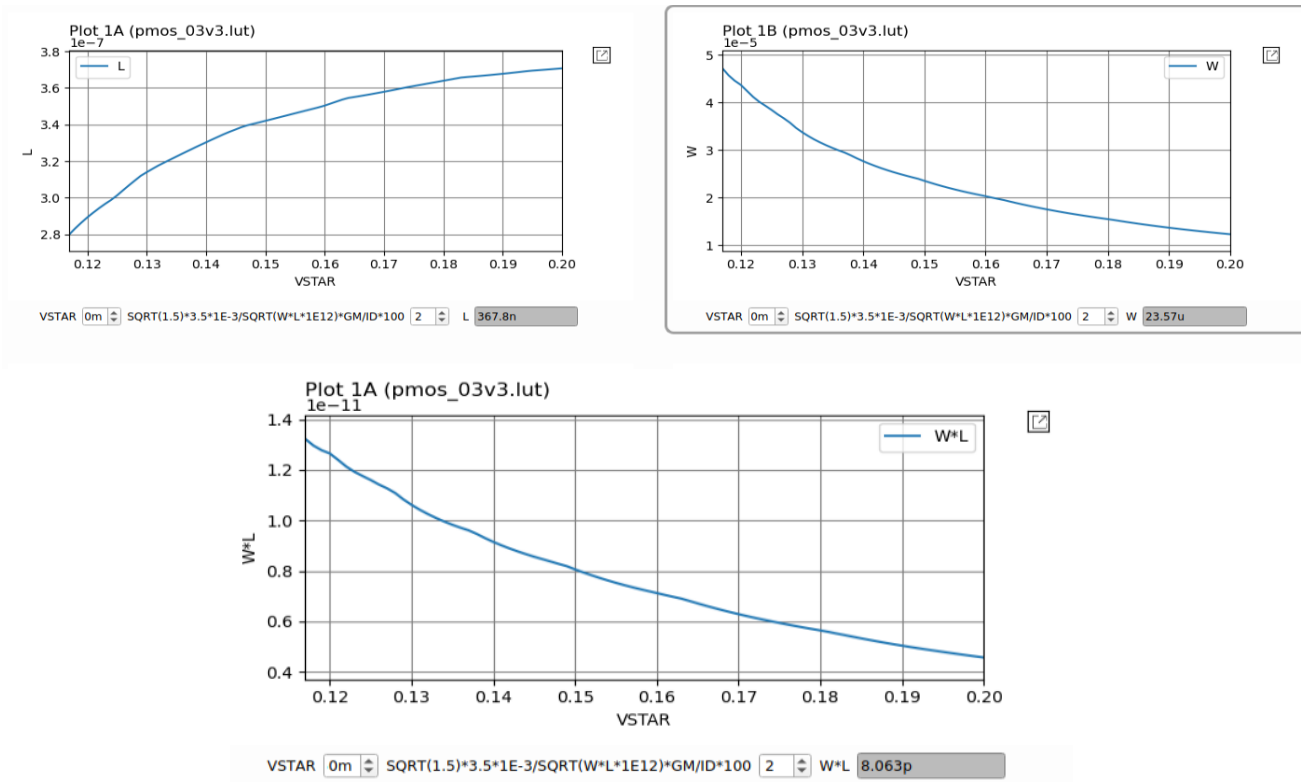
- ➔ ADT Hint: If the LUT contains mismatch data, we can directly use the parameter idmis in SA to get the standard deviation of the current random variations ' $\text{idmis_}\% = \text{sqrt}(1.5) * \text{idmis} / ID * 100$ '. The mismatch data can be added to any LUT using ADT by using an appropriate Monte Carlo mismatch model file.




- 11) As seen in the plot above, for a given mismatch requirement, the minimum area is achieved at the max V^* . Similarly, for a given area requirement, the minimum mismatch is achieved at the max V^* . That's why current mirrors are commonly biased in strong inversion.
- 12) The plot also shows that at a given V^* (compliance voltage), going for lower mismatch necessitates longer L , which also gives lower λ (higher r_o , although the effect of L on λ is limited at low V_{DS}). However, this comes at the expense of area.
- 13) Given the compliance voltage spec, **report** the above figure with a cursor added to the selected design point.
- 14) **Calculate** the min and max CM input levels. Is the previously selected CM input level in the valid range?

Part 2: Differential Amplifier Simulation

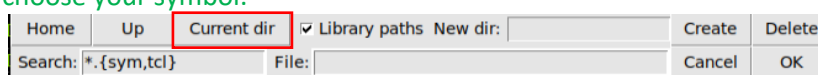- 1) Create the schematic of a differential amplifier "lab_06_diff_amp".
- 2) Create a symbol for the diff pair. Edit the symbol to look as shown below in the testbench schematic.
 - ➔ Xschem Hint: We will put the circuit under test in a schematic, create a symbol using hot key "A", then create a new schematic for the testbench.
 - ➔ Xschem Hint: To edit the symbol shape press file open then press current dir then choose your symbol -note you should choose <name>.sym to edit symbol-.
- 3) Create a new cell for the testbench "lab_06_diff_amp_tb". Create the testbench schematic as shown below.
 - ➔ Xschem Hint: To Place your symbol into the testbench use "Shift + I" then press current dir then choose your symbol.



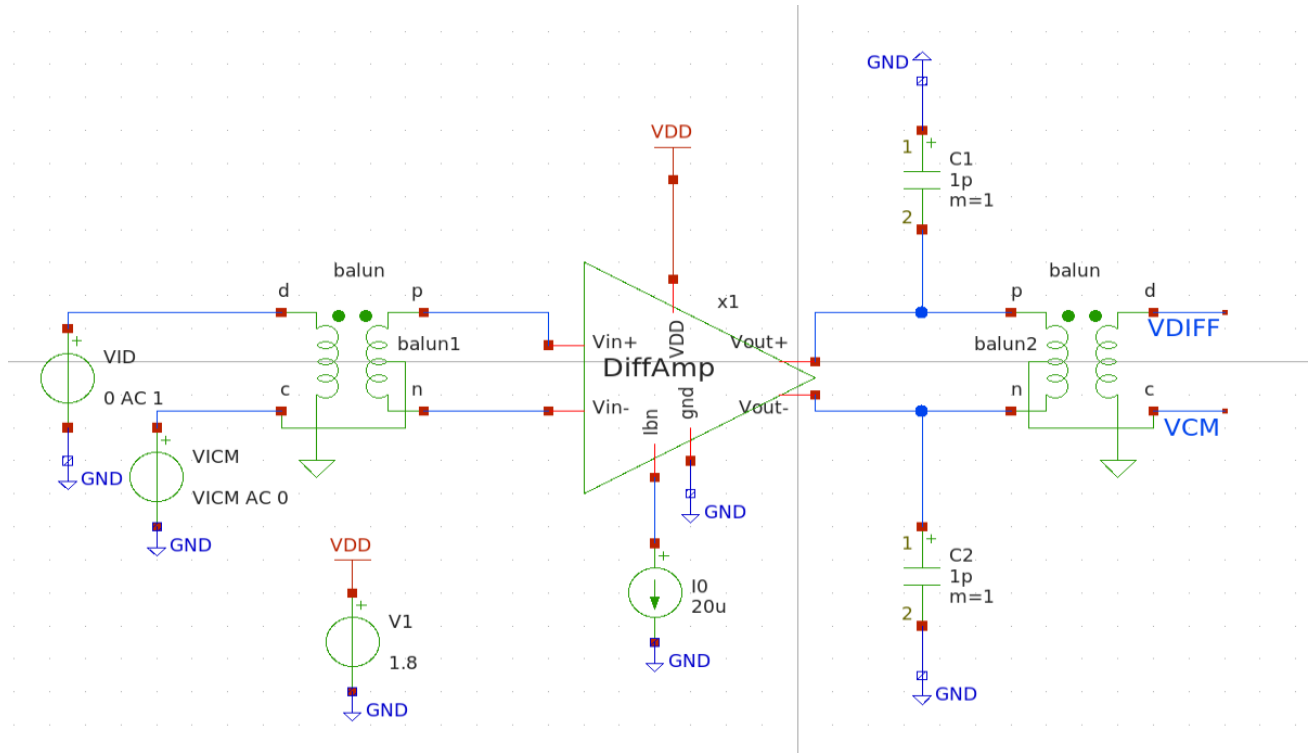

→ Xschem Hint: To add Balun:

1- download the following 3 files into your machine into the same folder as your schematic.

<https://drive.google.com/drive/folders/1CeNCPqHtC3S5WrG-pIEf9yIG7et6GVgo?usp=sharing>

2- Press "Shift + I" → current dir → balun.sym

3- Set the transistor sizing and Vicm as designed in Part 1. Unless otherwise stated, set Vid = 0 (this is the large signal differential input voltage).

NOTE: Use IB = 20uA (the CM multiplies this by 2, so each half in the diff pair gets IB).

Report the following:

1) OP simulation.

```
.control
save all
op
show m : id : gm : gds : vgs : vth : vds : vdsat
.endc
```

- Report a snapshot clearly showing the following parameters.

ID
VGS
VDS
VTH
VDSAT
GM
GDS
GMB
Region

- Check that all transistors operate in saturation.

2) Diff small signal ccs:

- Use AC magnitude = 1 for the diff source (and AC magnitude = 0 for the CM source).
- Run AC analysis (1Hz:10GHz, logarithmic, 10 points/decade).
- Report the Bode plot of small signal diff gain.
- Compare the DC diff gain and BW with hand analysis in a table.


```
.control
save all
op
ac dec 10 1 10G
meas ac Gain MAX vmag(VDIFF) FROM=1 TO=10G
let ff2=Gain*0.707
meas ac BW WHEN vmag(VDIFF)=ff2 FALL =1
save v(VDIFF)
remzerovec
write lab6_ac.raw
.endc
```

3) CM small signal ccs:

- Use AC magnitude = 1 for the CM source (and AC magnitude = 0 for the diff source).
- Run AC analysis (1Hz:10GHz, logarithmic, 10 points/decade).

```
.control
save all
op
ac dec 10 1 10G
meas ac CMGain MAX vmag(VCM) FROM=1 TO=1k
remzerovec
write lab6_ac.raw
.endc
```

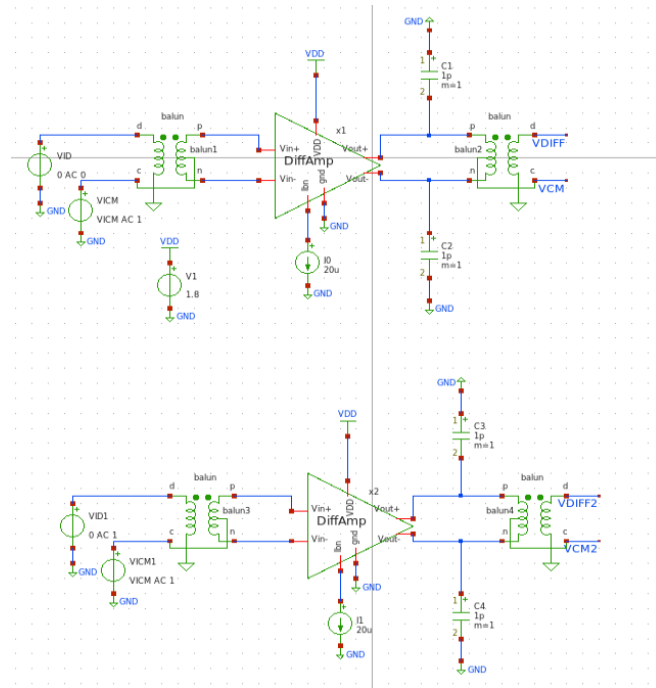- Report the Bode plot of small signal CM gain.
- Compare the DC CM gain with hand analysis in a table. Is it smaller than “1”? Why?
- Justify the variation of A_{vcm} vs frequency.
- Plot A_{vd}/A_{vcm} in dB. Compare A_{vd}/A_{vcm} @ DC with hand analysis in a table.



```
.control
save all
op
ac dec 10 1 1G
meas ac CMGain MAX vmag(VCM) FROM=1
TO=1MEG
meas ac DiffGain MAX vmag(VDIFF2) FROM=1
TO=1MEG
let CMRR_val = DiffGain / CMGain
print CMRR_val
let CMRR = v(VDIFF2) / v(VCM)
save CMRR
remzerovec
write lab6_ac_CM.raw
.endc
```

➔ Xschem Hint: To calculate CMRR we will use two duplicate of the design one with Diff in and the other with CM input.

- Justify the variation of A_{vd}/A_{vcm} with frequency.

CMRR is proportional to RSS and RSS decreases with frequency due to C_p

4) Diff large signal ccs:


- Use dc sweep (not parametric sweep) for $V_{id} = -V_{DD}:10m:V_{DD}$.

```

.control
save all
dc VID -1.8 1.8 0.1
let VDIFF_real= Vpos - Vneg
save VDIFF_real
plot VDIFF_real
remzerovec
write lab6_ID.raw
.endc

```

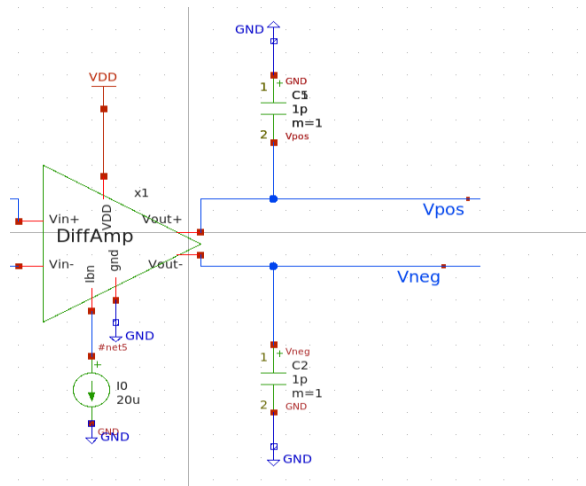➔ Xschem Hint: in the following parts we need to remove the output Balun and rename the output nodes.



- Report diff large signal ccs (VODIFF vs VIDIFF). Compare the extreme values with hand analysis in a table.

5) CM large signal ccs (GBW vs Vicm):

```
.control
let Vstart=0
let Vstop=1.8
let Vstep=10m
let Vact=Vstart
let VICMmax=0
let VICMmin =0
save all
while Vact le Vstop
  alter VICM Vact
  ac dec 10 1 100G
  let vx = Vpos - Vneg
  meas ac DiffGain MAX vx FROM=1 TO=100MEG
  let ff1=DiffGain*0.707
  meas ac f3db WHEN vx = ff1 FALL =1
  let GBW = DiffGain*f3db
  save GBW
  let vx = Vact
  let VICMact = Vact + VICM
  save VICMact
  set appendwrite
  remzerovec
  write Lab6_param.raw


  if (GBW > 27MEG)
    let VICMmax = Vact
  endif

  if (GBW < 27MEG)
    if (Vact<0.5)
      let VICMmin = Vact
    endif
  endif

  let Vact=Vact+Vstep
end
print VICMmax
print VICMmin
.endc
```

- We will use parametric sweep on AC analysis to get GBW.
- Report CM large signal ccs (GBW vs VICM). Assume the valid range for Vicm (CMIR) is defined by the condition that Avd is within 90% of the max gain, i.e., 10% drop in gain.
- Find the CM input range (CMIR). Compare with hand analysis in a table.

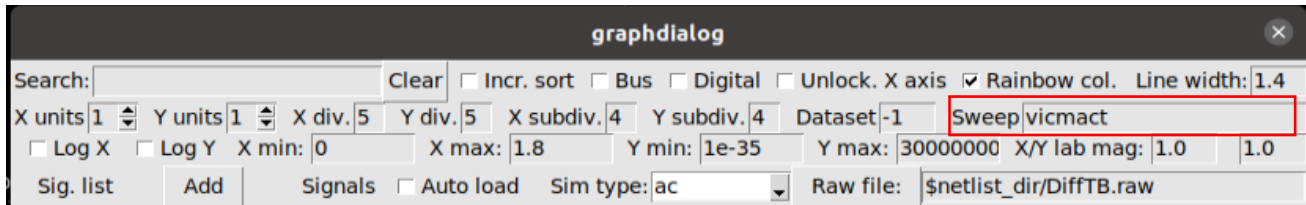- Xschem Hint: To plot gbw vs VICMact write in sweep VICMact. Note that you can plot vs Vx both stores VICM values.



Lab Summary

- In Part 1 you learned:
 - How to design a resistive-loaded differential amplifier.
- In Part 2 you learned:
 - How to use an ideal balun to test a differential amplifier.
 - How to simulate the small-signal differential gain of a differential amplifier.
 - How to simulate the small-signal common-mode gain of a differential amplifier.
 - How to simulate the large-signal differential characteristics of a differential amplifier.
 - How to simulate the large-signal common-mode characteristics of a differential amplifier.

Acknowledgements

Thanks to all who contributed to these labs. Special thanks to Dr. Sameh A. Ibrahim for reviewing and editing the labs. If you find any errors or have suggestions concerning these labs, please contact Hesham.omran@eng.asu.edu.eg.