

ITI CMOS Analog IC Design 2024
Lab 03
Cascode Amplifier

PART 1: Sizing Chart

1. $|Av| \approx gmro = 2I_D/V_{ov} \times V_A / I_D = 2V_A / V_{ov}$
 - if we compute V_{ov} and $2I_D/gm$ they will not be equal. Let's define a new parameter called V-star (V^*) which is calculated from actual simulation data using the formula $V^* = 2I_D/gm \leftrightarrow gm = 2I_D / V^*$
2. The specs we must achieve.

spec	Value
gm*ro	50
gm/Id	10
Supply	1.8V
Quiescent (DC) output voltage	$V_{DD} / 2 = .9$
Current consumption	20μA

ID	20u	?
gm/ID	10	?
gm/gds	50	?
VDS	0.9	?
VSB	0	?

Results:

Name		TT-27.0
2	IG	N/A
3	L	330n
4	W	3.32u
5	VGS	793.1m
6	VDS	900m

- From SA in ADT we need NMOS with $L=330\text{nm}$ and $W=3.32\mu\text{m}$ and the voltage in gate $V_{GS}=793.1\text{ mV}$ to achieve the specs above

M1

LUT ?

Corner ☐ All ?

Temp (°C) ☐ All ?

Frequency ?

Stack ?

ID ?

W ?

L ?

VDS ?

VSB ?

Results:

	Name	TT-27.0
4	W	3.32u
5	VGS	804m
6	VDS	450m
7	VSB	0
8	gm/ID	9.741

M2

LUT ?

Corner ☐ All ?

Temp (°C) ☐ All ?

Frequency ?

Stack ?

ID ?

W ?

L ?

VDS ?

VSB ?


Results:

	Name	TT-27.0
4	W	3.32u
5	VGS	909.8m
6	VDS	450m
7	VSB	450m
8	gm/ID	9.618

- $V_B = V_{GS2} + V_{DS1} = 909.8 + 450 = 1359 \text{ mV}$

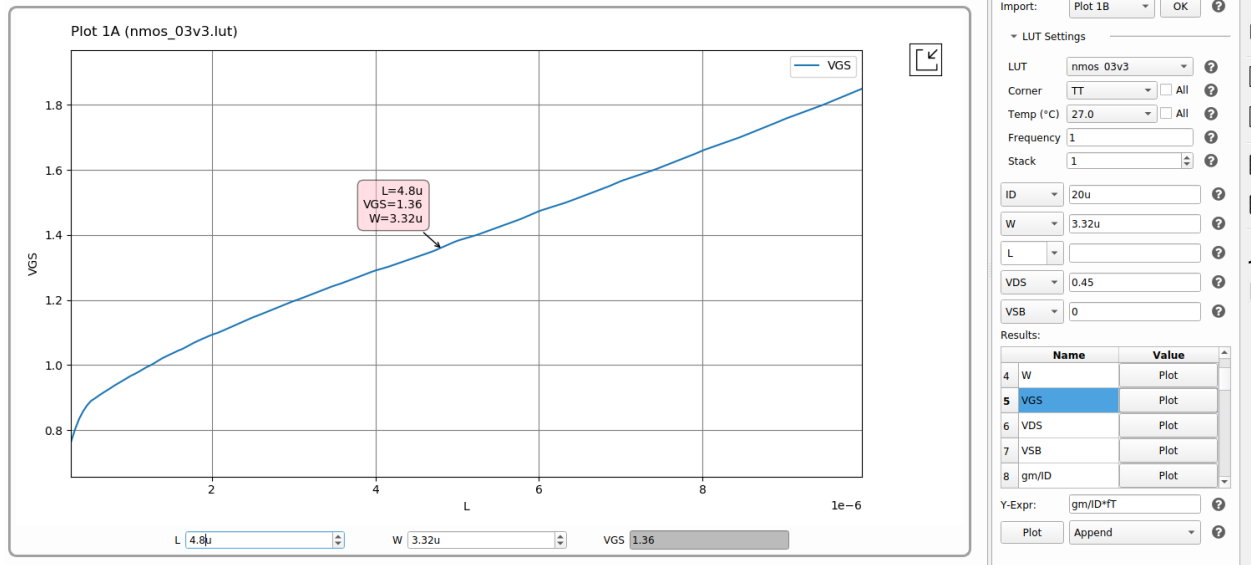4. M3 and M4 are used to generate the Cascode bias voltage.

- find L_3 at $V_{GS} = V_B = V_{GS2} + V_{DS1}$ using W_3, I_D .



- $L_3 = 4.8 \mu\text{m}$

5. Simulate the DC OP point of the CS and cascode amplifiers.

```

igain0 = 4.707964e+01
igain1 = 1.445516e+03
binary raw file "lab3.raw"
BSIM4v5: Berkeley Short Channel IGFET Model-4
  device      m.xm3.m0      m.xm4.m0      m.xm2.m0
  model      nmos_3p3.10    nmos_3p3.8    nmos_3p3.8
  id          2e-05         2e-05         2e-05
  vgs         1.36366       0.903809      0.912647
  vth         0.65495       0.774616      0.777992
  vds         0.45984       0.903801      0.450764
  vdsat       0.549665      0.164476      0.168102
  gm          4.5658e-05     0.000198379   0.000195411
  gds         1.2877e-05     4.55058e-06   5.83296e-06
  gmbs        1.77078e-05    4.09775e-05   4.08803e-05
  cdb         -8.21134e-15    -1.99345e-16  -2.05408e-16
  cgd         -4.55802e-15    2.52964e-17   2.00481e-17
  cgs         -4.493e-14     -2.36965e-15  -2.39635e-15
  csb         -1.08115e-14    -2.98619e-16  -3.05644e-16

BSIM4v5: Berkeley Short Channel IGFET Model-4
  device      m.xm1.m0      m.xm0.m0
  model      nmos_3p3.8    nmos_3p3.8
  id          2e-05         2e-05
  vgs         0.805788      0.790787
  vth         0.673713      0.664441
  vds         0.451001      0.89768
  vdsat       0.164544      0.160739
  gm          0.000196097    0.000199096
  gds         5.49551e-06    4.22893e-06
  gmbs        5.35701e-05    5.40377e-05
  cdb         -2.67481e-16    -2.61376e-16
  cgd         1.43821e-17     1.94041e-17
  cgs         -2.34049e-15    -2.31133e-15
  csb         -3.98066e-16    -3.9154e-16

```

- PS. I change the code to make Vth before Vds to make Vds before Vdsat to make it easier to notice is that in saturation or not.

6. Putting the OP of all transistors in a table with the appropriate units

device	M0	M1	M2	M3	M4
id	20 μA	20 μA	20 μA	20 μA	20 μA
vgs	796.84 mV	812.11 mV	908.43 mV	1361.08 mV	896.59 mV
vth	670.42 mV	679.97 mV	773.82 mV	653.73 mV	767.49 mV
vds	903.73 mV	455.52 mV	447.22 mV	464.47 mV	896.58 mV
vdsat	160.81 mV	164.62 mV	168.06 mV	548.63 mV	164.39 mV
gm	199.01 μS	196.05 μS	195.44 μS	46.13 μS	198.5 μS
Gds	4.22 μS	5.46 μS	5.86 μS	12.17 μS	4.56 μS
Gmbs	54.01 μS	53.56 μS	40.85 μS	17.85 μS	40.91 μS
Cdb	-261.37 aF	-267.42 aF	-205.29 aF	-8148.73 aF	-198.89 aF
Cgd	19.42 aF	14.58 aF	19.9 aF	-4302.41 aF	25.34 aF
Cgs	-2.31 fF	-2.34 fF	-2.4 fF	-44.98 fF	-2.37 fF
Csb	-391.54 aF	-398.05 aF	-304.88 aF	-10793.8 aF	-298.05 aF
1.2*vdsat	192.98 mV	197.54 mV	201.67 mV	658.36 mV	197.27 mV

7. Check that all transistors operate in saturation. **Check $V_{DS} > V_{dsat} * 1.2$**

- For M0: **903.73 mV > 192.98 mV** then it's in **Saturation**
- For M1: **455.52 mV > 197.54 mV** then it's in **Saturation**
- For M2: **447.22 mV > 201.67 mV** then it's in **Saturation**
- For M3: **464.47 mV < 658.36 mV** then it's in **Triode**
- For M4: **896.58 mV > 197.27 mV** then it's in **Saturation**
 - M3 works in triode: as M3 has low aspect ratio than any other NMOS it has higher $V_{GS} = 1361.08 \text{ mV}$ than anyone, so it has higher $V_{ov} \approx V_{dsat} * 1.2 = 658.36 \text{ mV}$ too and as M4 is diode connected and suffer from body effect, so it has high V_{th} , so it consumes 896.59 mV from V_{GSQ3} and let $1361.08 - 896.59 = 464.49 \text{ mV}$ and it's less than V_{ov} to make M3 work in saturation

8. Approximately, M0, M1 and M3 has the same V_{th} but M4 and M2 has higher V_{th} because they suffer from body effect as there are a voltage difference between their source and body terminal.


- As M0 and M1 has the same V_{th} and has the same I_D and aspect ratio they have the same V_{GS}

9. In all transistor $gm \gg gds$. But for M3: $gm > gds$ because it is on triode and has low r_o and then high gds

10. In all transistor $g_m > g_{mb}$ as $g_{mb}/g_m \approx .3-.4$
11. In all transistor $|c_{gs}| \gg |c_{gd}|$ as
12. In all transistor $|c_{sb}| > |c_{db}|$ as $|c_{db}|/|c_{sb}| \approx .67$

2. AC Analysis

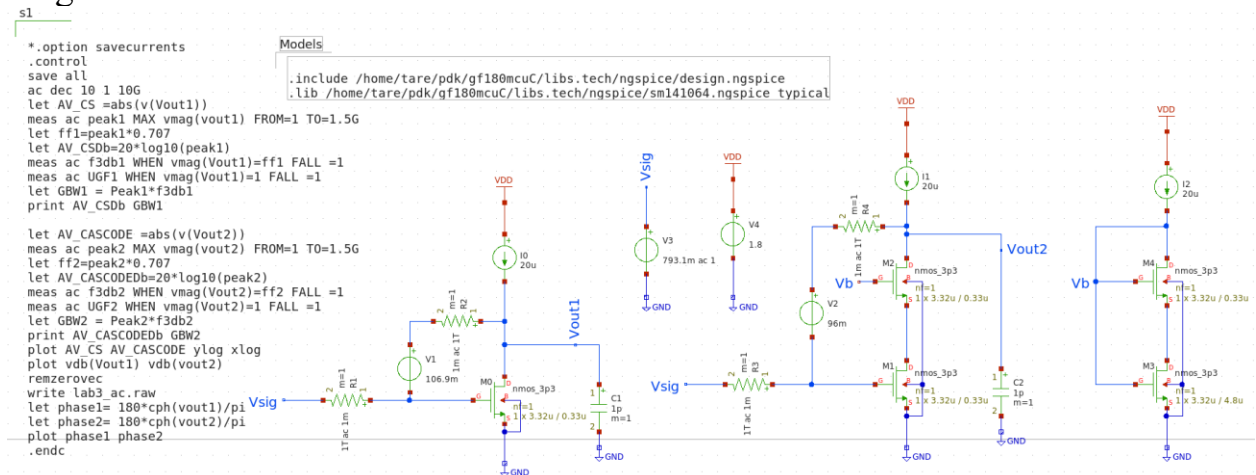1. Perform AC analysis (1Hz:10GHz, logarithmic, 10points/decade) to simulate gain and bandwidth.



2. expressions for circuit parameters (DC gain, BW, GBW, and UGF) and export them to interactive.


```

peak1           = 4.723033e+01 at= 1.000000e+00
f3db1           = 6.701949e+05
ugf1            = 3.156219e+07
av_csdb         = 3.348442e+01
gbw1            = 3.165353e+07
peak2           = 1.507056e+03 at= 1.000000e+00
f3db2           = 2.016317e+04
ugf2            = 3.057482e+07
av_cascodeb     = 6.356259e+01
gbw2            = 3.038703e+07


```


3. Bode plot (magnitude) of CS and cascode appended on the same plot.

3.1. Magnitude

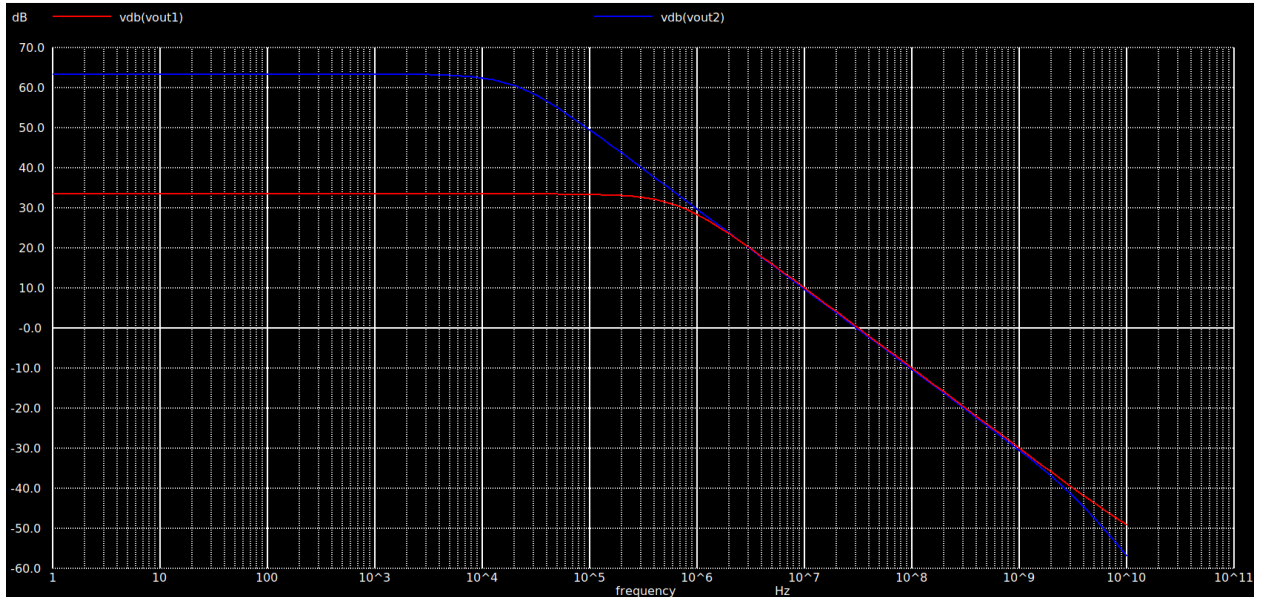

3.2. Phase

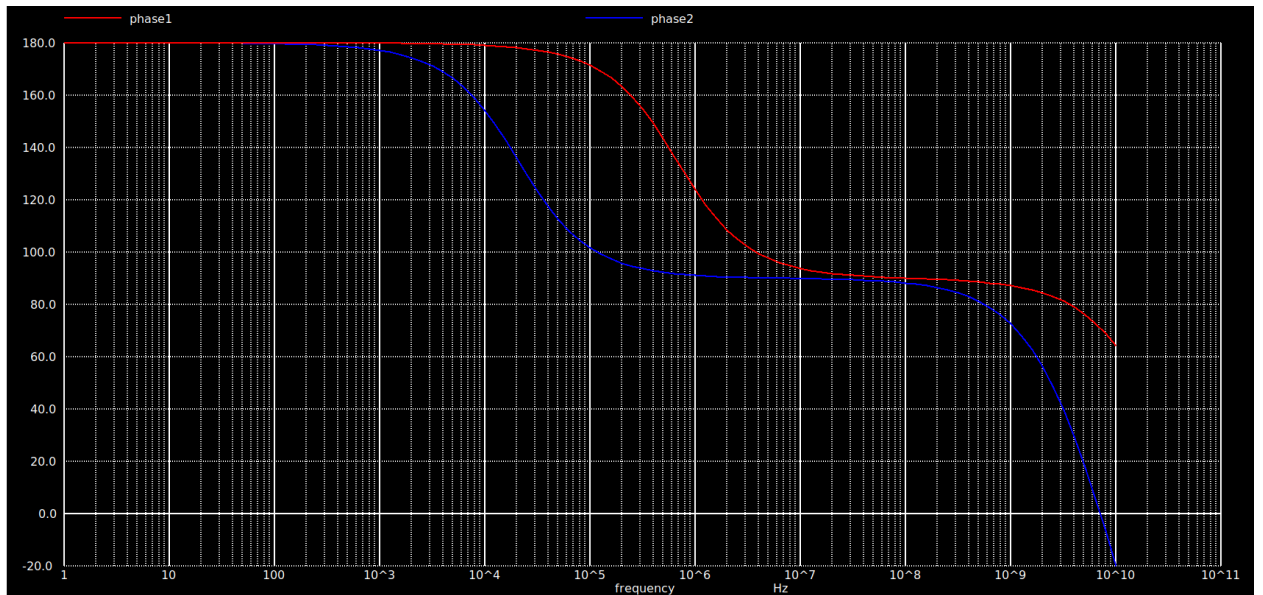

$$4. \text{ Dc gain for Common source(M0) amplifier} = -\frac{gm}{1+(gm+gmb)Rs} * ro = -\frac{gm}{gds}$$

$$= -199.01 \mu S / 4.22 \mu S = -47.16$$

$$- \text{ Dc gain for Cascode amplifier} = -\frac{gm1}{1+(gm1+gmb1)Rs2} * ro1 * (gm2 + gmb2)ro2 = -\frac{gm1}{gds1} * \frac{gm2+gmb2}{gds2} = -1481.3$$

- Bandwidth for CS Amplifier as from the bode plot we can notice that the output pole is the dominant $f_c = \frac{1}{2\pi R_{out}(C_L + C_{db} + C_{gd})} = \frac{1}{2\pi(263.97e3(1e-12 + 19.42e-18 + 261.37e-18))} = 603 \text{ KHz}$
- For Cascode Amplifier the output pole is the dominant $f_c = \frac{1}{2\pi R_{out}(C_L + C_{db} + C_{gd})} = \frac{1}{2\pi(7.56e6(1e-12 + 19.9e-18 + 205.29e-18))} = 21 \text{ kHz}$
- GainBandWidth Product for CS, $GBW = f_c * A_v = 603 * 10^3 * 47.16 = 28.44 * 10^6$
- GainBandWidth Product for Cascode, $GBW = f_c * A_v = 21 * 10^3 * 1481 = 28.44 * 10^6 = 31 * 10^6$
- Unity gain frequency $UGF = GBW$

5. table comparing the DC gain, BW, UGF, and GBW of CS Amplifier.

CS Amplifier	DC gain	BW	UGF	GBW
Simulation	47.23	670.19 kHz	31.56 MHz	31.65 MHz
Analytical	47.16	603 kHz	28.44 MHz	28.44 MHz

- table comparing the DC gain, BW, UGF, and GBW of Cascode Amplifier

Cascode Amplifier	DC gain	BW	UGF	GBW
Simulation	1507	21.16 kHz	30.57 MHz	30.39 MHz
Analytical	1481	21 kHz	31 MHz	31 MHz

6. we notice that GBW for CS and Cascode are approximately the same as Cascode amplify the R_{out} but reduce the Bandwidth
- we see that cascode amplifier has very high gain but less bandwidth
 - the cascode has less swing for output and must bias V_B to has value bigger than $V_{ov1} + V_{ov2} + V_{th2}$

3. Simulate the DC OP point of the new CS and cascode amplifiers.

```

igain0 = 4.403117e+01
igain1 = 1.580814e+03
binary raw file "lab3.raw"
BSIM4v5: Berkeley Short Channel IGFET Model-4
  device      m.xm3.m0      m.xm5.m0      m.xm4.m0
  model      nmos_3p3.10    nmos_3p3.8    nmos_3p3.8
  id         2e-05         2e-05         2e-05
  vgs        1.36366       0.803448      0.899981
  vds        0.463659      0.803441      0.899974
  vth        0.655911      0.675868      0.770838
  vdsat      0.548938      0.161599      0.164434
  gm         4.602e-05      0.000198559   0.000198448
  gds        1.23028e-05     4.33626e-06   4.55847e-06
  gmbs       1.78233e-05     5.39715e-05   4.09126e-05
  cdb        -8.16058e-15    -2.62358e-16  -1.98966e-16
  cdg        -2.00346e-14    -9.48214e-16  -9.57814e-16
  cgs        -4.497e-14      -2.31725e-15  -2.36981e-15
  csb        -1.07937e-14    -3.92847e-16  -2.98047e-16

BSIM4v5: Berkeley Short Channel IGFET Model-4
  device      m.xm2.m0      m.xm1.m0      m.xm0.m0
  model      nmos_3p3.8      nmos_3p3.8      nmos_3p3.8
  id         1.88613e-05     1.88613e-05     2.34426e-05
  vgs        0.903329       0.803449       0.803447
  vds        0.490903       0.460312       0.745066
  vth        0.775275       0.677347       0.659037
  vdsat      0.16365        0.160586       0.172757
  gm         0.000189593     0.000189808     0.000216885
  gds        5.3144e-06      5.17462e-06     4.92571e-06
  gmbs       3.94414e-05     5.18304e-05     5.90354e-05
  cdb        -2.02031e-16     -2.65133e-16    -2.68353e-16
  cdg        -9.61542e-16     -9.52201e-16    -9.71288e-16
  cgs        -2.37211e-15     -2.3181e-15     -2.37788e-15
  csb        -3.01172e-16     -3.94816e-16    -4.0164e-16

```

- PS) I change the order and make Vth before Vds and vdsat
- 4. From figure above we can notice that $v_{ds} > v_{dsat}$ for all transistor but M3 which has $v_{ds} < v_{dsat}$ so all transistor work in saturation but M3 works in triode
- M3 works in triode: as M3 has low aspect ratio than any other NMOS it has higher V_{GS} than anyone, so it has higher $V_{ov} \approx V_{dsat} * 1.2 = 658.78 \text{ mV}$ too and as M4 is diode connected and suffer from body effect, so it has high V_{th} , so it consumes 900.76 mV from V_{GSQ3} and let $1364.44 - 900.76 = 463.68 \text{ mV}$ and it's less than V_{ov} to make M3 work in saturation

2. AC Analysis


1. Performing AC analysis (1Hz:10GHz, logarithmic, 10points/decade) to simulate gain and bandwidth

2. create expressions for circuit parameters (DC gain, BW, GBW, and UGF)


```
peak1          = 7.341043e+00 at= 1.000000e+00  
f3db1          = 1.928633e+06  
ugf1           = 1.418322e+07  
av_csdb       = 1.731516e+01  
gbw1          = 1.415818e+07  
peak2          = 8.551252e+00 at= 1.000000e+00  
f3db2          = 3.243251e+06  
ugf2           = 2.781260e+07  
av_cascodeb   = 1.864059e+01  
gbw2          = 2.773386e+07
```

3. Bode plot (magnitude) of CS and cascode **appended on the same plot.**

3.1. magnitude

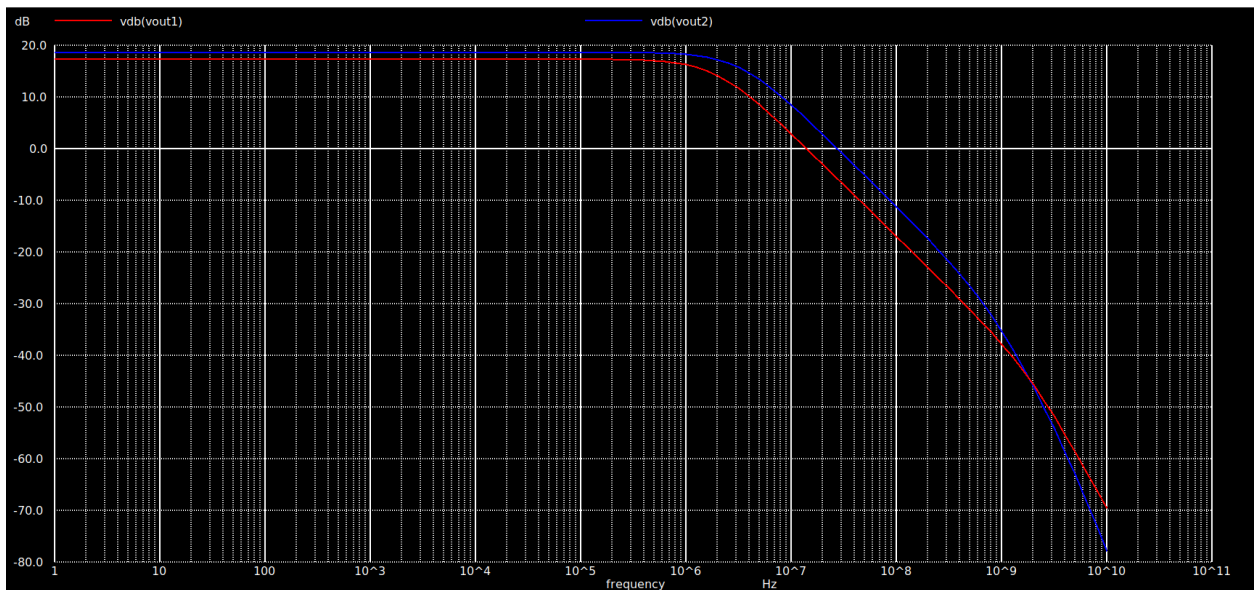

3.2. phase

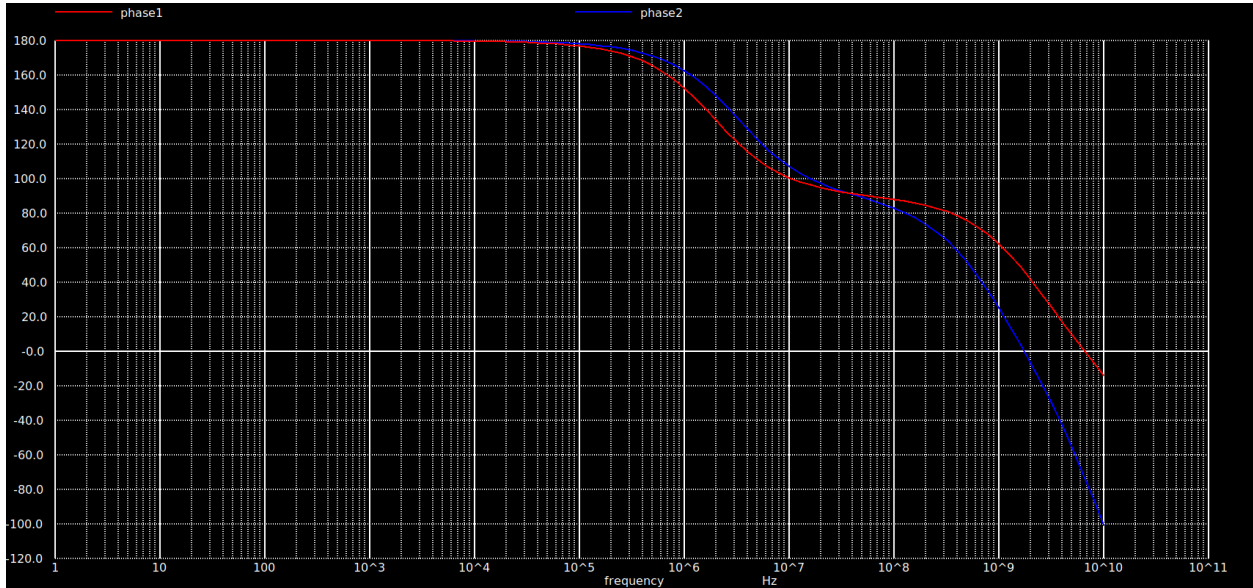

4. Dc gain for Common source(M0) amplifier = -
 $gm/(1+(gm+gmb)Rs)*(ro||R_D) = -gm*(R_D||1/gds) = -7.77$
 - Dc gain for Cascode amplifier = $gm1 * (ro2 * (1 + (gm2 + gmb2)ro1))||RD \approx -gm1 * RD = -8.67$
 - Bandwidth for CS Amplifier as from the bode plot we can notice that the input pole is the dominant $fc = \frac{1}{2\pi Rin((1+Av)cdg+cgs)} = 1.46MHz$
 - For Cascode Amplifier the output pole is the dominant

$$fc = \frac{1}{2\pi Rin(2cdg1 + cgs1)} = 3.77 MHz$$
 - GainBandWidth Product for CS, $GBW = fc * Av = 11.34 MHz$
 - GainBandWidth Product for Cascode, $GBW = fc * Av = 32.69 MHz$
 - Unity gain frequency $UGF = GBW$
5. table comparing the DC gain, BW, UGF, and GBW of CS Amplifier.

CS Amplifier	DC gain	BW	UGF	GBW
Simulation	7.34	1.93 MHz	14.18 MHz	14.16 MHz
Analytical	7.77	1.46 MHz	11.34 MHz	11.34MHz

- table comparing the DC gain, BW, UGF, and GBW of Cascode Amplifier.

Cascode Amplifier	DC gain	BW	UGF	GBW
Simulation	8.55	3.24 MHz	27.81 MHz	27.73 MHz
Analytical	8.67	3.77 MHz	32.69 MHz	32.69MHz

6. we notice that GBW for Cascode bigger than CS amplifier when input pole is dominant, and they are equal when the output pole is dominant
 - we see that cascode amplifier has slightly higher gain than CS because of the high increase in R_{out} and high Bandwidth because of the cascode decrease miller effect in the input capacitance
 - as the input pole has lower value than the output pole in part 2 the bandwidth in part 3 is less than the bandwidth in part 2