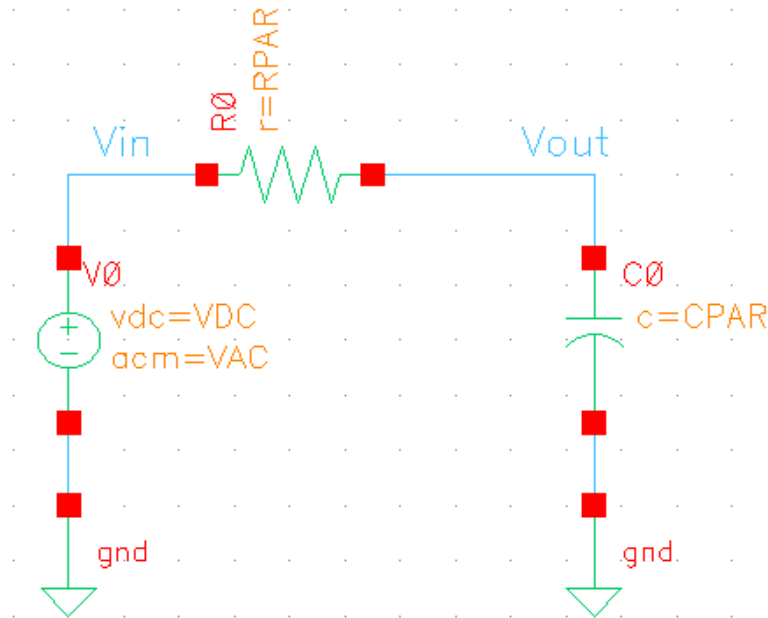



ITI CMOS Analog IC Design 2024
Lab 10
Noise Simulation

PART 1: LPF AC Noise Analysis

1. Schematic



2. Plotting output noise vs frequency.

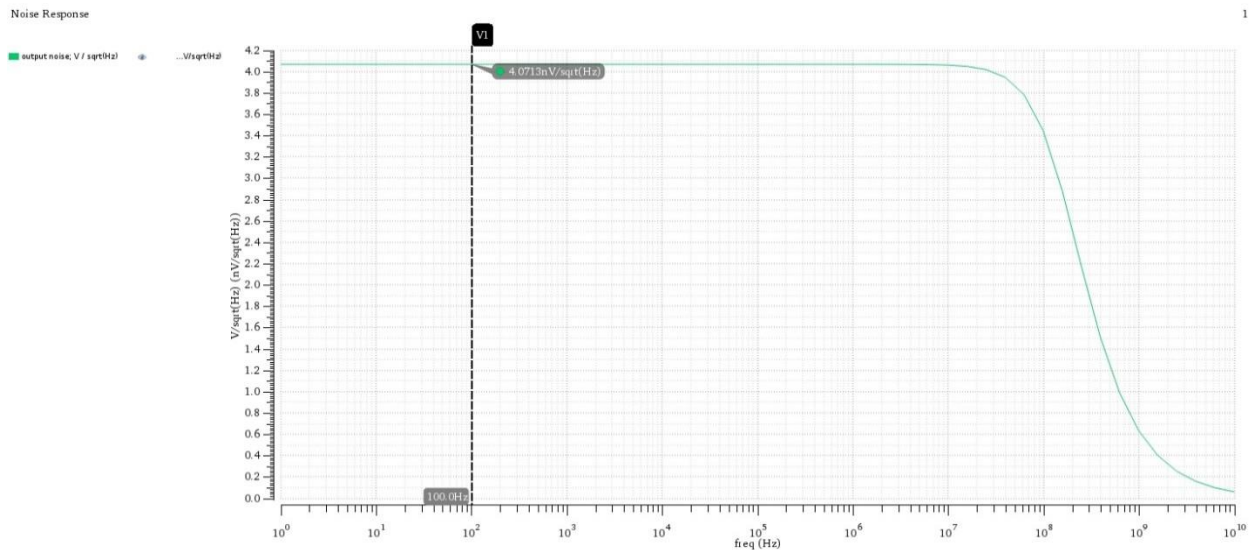

3. Bandwidth, RMS value, and density from calculator

| ITL_Su2024:lab10_LPF:1 | density | 4.071n |
|------------------------|---------|--------|
| ITL_Su2024:lab10_LPF:1 | BW | 158.8M |
| ITL_Su2024:lab10_LPF:1 | rms | 65.16u |

4. Hand analysis for density, bandwidth, and RMS value


$$V_n = \sqrt{\frac{R}{1k}} * 4 \frac{nV}{\sqrt{Hz}} = \sqrt{\frac{1k}{1k}} * 4 \frac{nV}{\sqrt{Hz}} = 4 \frac{nV}{\sqrt{Hz}}$$

$$BW = \frac{1}{2\pi RC} = \frac{1}{2\pi * 1k\Omega * 1pF} = 159.155MHz$$

$$V_{nrms} = \sqrt{\frac{1pF}{C}} * 64 \mu V = \sqrt{\frac{1pF}{1pF}} * 64 \mu V = 64\mu V$$

| | Simulation | Analysis |
|---------------------------------|------------------------------|--------------------------|
| Density V_n | $4.071 \frac{nV}{\sqrt{Hz}}$ | $4 \frac{nV}{\sqrt{Hz}}$ |
| BW | 158.8MHz | 159.155MHz |
| V_{nrms} | 65.16μV | 64μV |

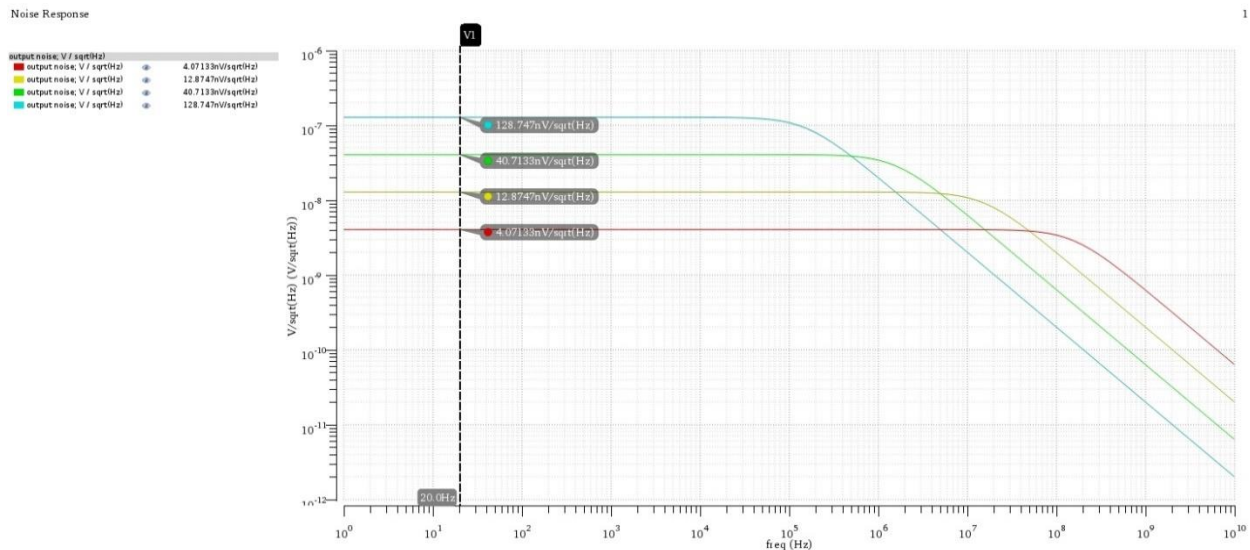5. Plotting output noise for RPAR = 1k, 10k, 100k, 1000k



- Bandwidth decreasing with increasing of resistor
- The density of noise increase with increasing of resistor


6. Bandwidth, RMS value, and density from calculator

| Parameters: RPAR=1k | | | |
|-----------------------|------------------------|---------|--------|
| 1 | ITI_Su2024:lab10_LPF:1 | Density | 4.071n |
| 1 | ITI_Su2024:lab10_LPF:1 | BW | 158.8M |
| 1 | ITI_Su2024:lab10_LPF:1 | RMS | 64.32u |
| Parameters: RPAR=10k | | | |
| 2 | ITI_Su2024:lab10_LPF:1 | Density | 12.87n |
| 2 | ITI_Su2024:lab10_LPF:1 | BW | 15.88M |
| 2 | ITI_Su2024:lab10_LPF:1 | RMS | 64.62u |
| Parameters: RPAR=100k | | | |
| 3 | ITI_Su2024:lab10_LPF:1 | Density | 40.71n |
| 3 | ITI_Su2024:lab10_LPF:1 | BW | 1.588M |
| 3 | ITI_Su2024:lab10_LPF:1 | RMS | 64.65u |
| Parameters: RPAR=1M | | | |
| 4 | ITI_Su2024:lab10_LPF:1 | Density | 128.7n |
| 4 | ITI_Su2024:lab10_LPF:1 | BW | 158.8k |
| 4 | ITI_Su2024:lab10_LPF:1 | RMS | 64.66u |

- V_{nrms} doesn't change with change of resistor
- $V_n \propto R$, and $BW \propto \frac{1}{R}$ so as R increase V_n increase but BW decrease so V_{nrms} remain constant

PART 2: LPF Transient Noise Analysis

1. Plotting the noise output waveform

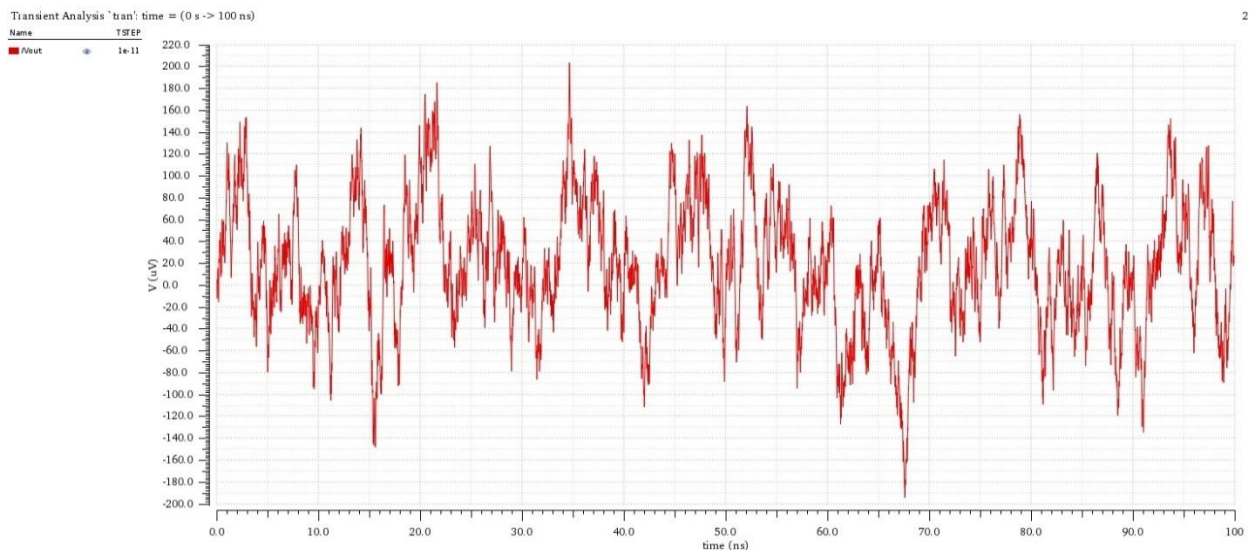


2. Annotate the min, max, and RMS values.

| | | |
|------------------------|-----|---------|
| ITI_Su2024:lab10_LPF:1 | rms | 60.88u |
| ITI_Su2024:lab10_LPF:1 | MAX | 203.8u |
| ITI_Su2024:lab10_LPF:1 | MIN | -194.2u |

- The RMS value is approximately equal to this of part 1

| | Part 1 | Part 2 |
|-----------|--------------|--------------|
| V_{rms} | $65.16\mu V$ | $60.88\mu V$ |

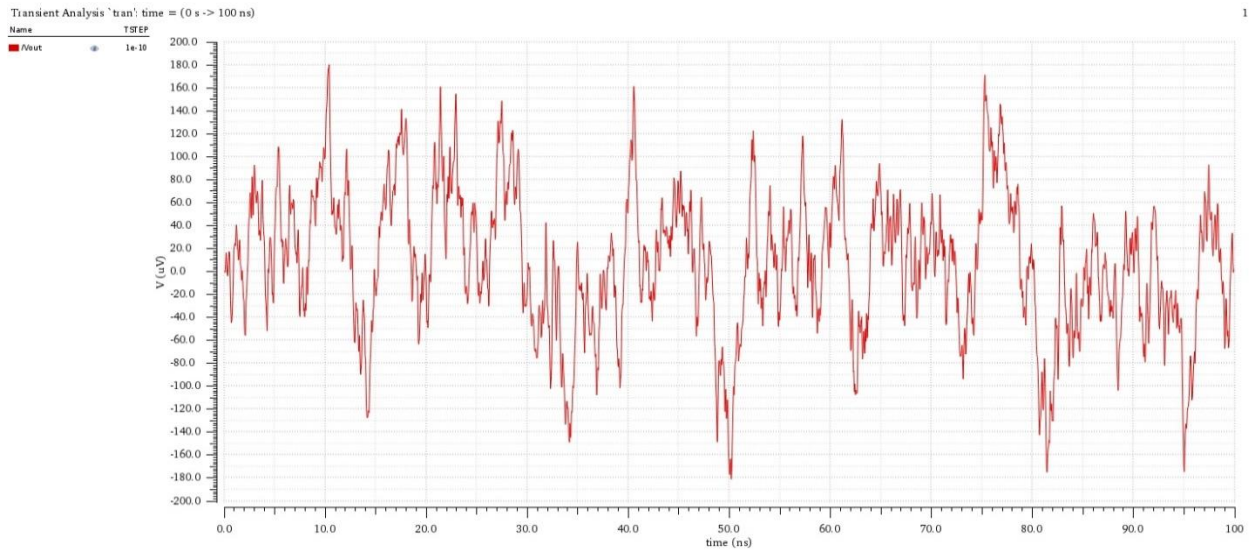- Repeat the simulation with TSTEP = TAU/10




- Annotate the min, max, and RMS values.

| | | |
|------------------------|-----|--------|
| ITI_Su2024:lab10_LPF:1 | rms | 61.59u |
| ITI_Su2024:lab10_LPF:1 | MAX | 180.2u |
| ITI_Su2024:lab10_LPF:1 | MIN | -181u |

- There is a bug in simulation as we increase TSTEP it decreases Fmax of noise analysis and step increase so we take less time of samples, and this decrease the accuracy and this should make the result decrease not increase.

5. Plotting the rms noise vs iteration

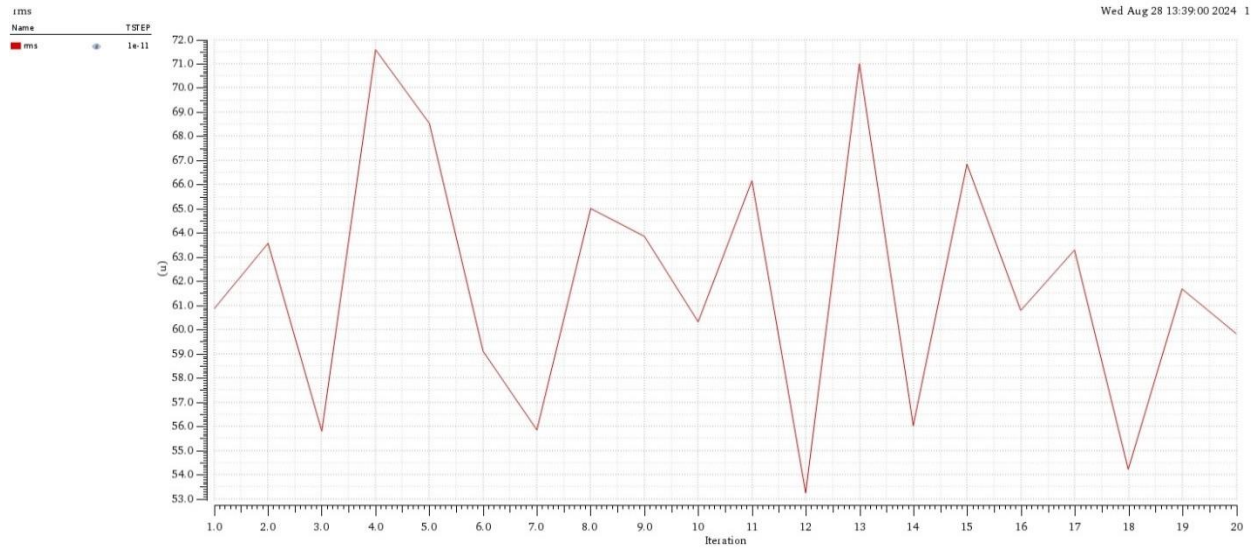


- Calculate the average rms noise

| | | |
|------------------------|---------|--------|
| ITI_Su2024:lab10_LPF:1 | average | 61.97u |
|------------------------|---------|--------|

| | Part 1 | Part 2 | Average |
|------------|---------------|---------------|---------------|
| V_{nrms} | 65.16 μV | 60.88 μV | 61.97 μV |

PART 3: 5T OTA AC Noise Analysis

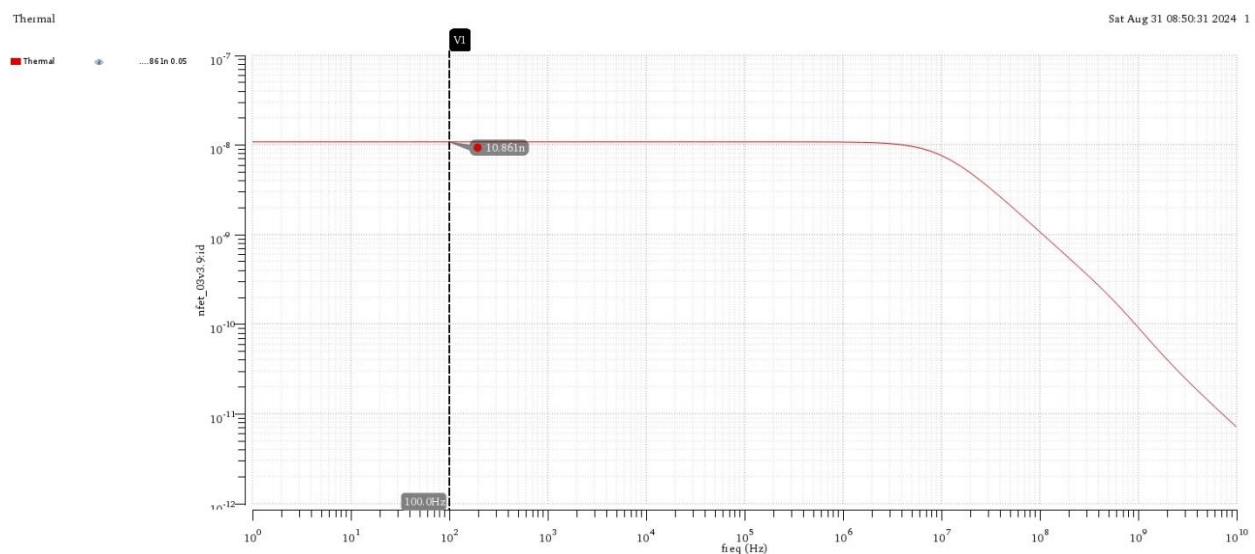1. Plotting output thermal noise vs frequency



2. Annotate noise density and bandwidth in the plot

| | | |
|------------------------|---------|--------|
| ITI_Su2024:5T_OTA_tb:1 | density | 10.86n |
| ITI_Su2024:5T_OTA_tb:1 | BW | 10.11M |


- Hand analysis for density and bandwidth

$$V_{nin} = \sqrt{\frac{8kT\gamma}{g_{m1,2}} \left(1 + \frac{g_{m3,4}}{g_{m1,2}}\right)} = \sqrt{\frac{8 \cdot 4.14 \cdot 10^{-21} J^{\frac{2}{3}}}{320 \mu S} \left(1 + \frac{216.5 \mu S}{320 \mu S}\right)} = 10.76 \frac{nV}{\sqrt{Hz}}$$


$$BW = GBW_{OL} = \frac{g_{m2}}{2\pi * C_L} = \frac{320.25 \mu S}{2\pi * 5 pF} = 10.19 MHz$$

| | Simulation | Analysis |
|---------------------------------|------------------------------|------------------------------|
| Density V_n | $10.86 \frac{nV}{\sqrt{Hz}}$ | $10.76 \frac{nV}{\sqrt{Hz}}$ |
| BW | 10.11MHz | 10.19MHz |


- Flicker noise as y-axis is log scale

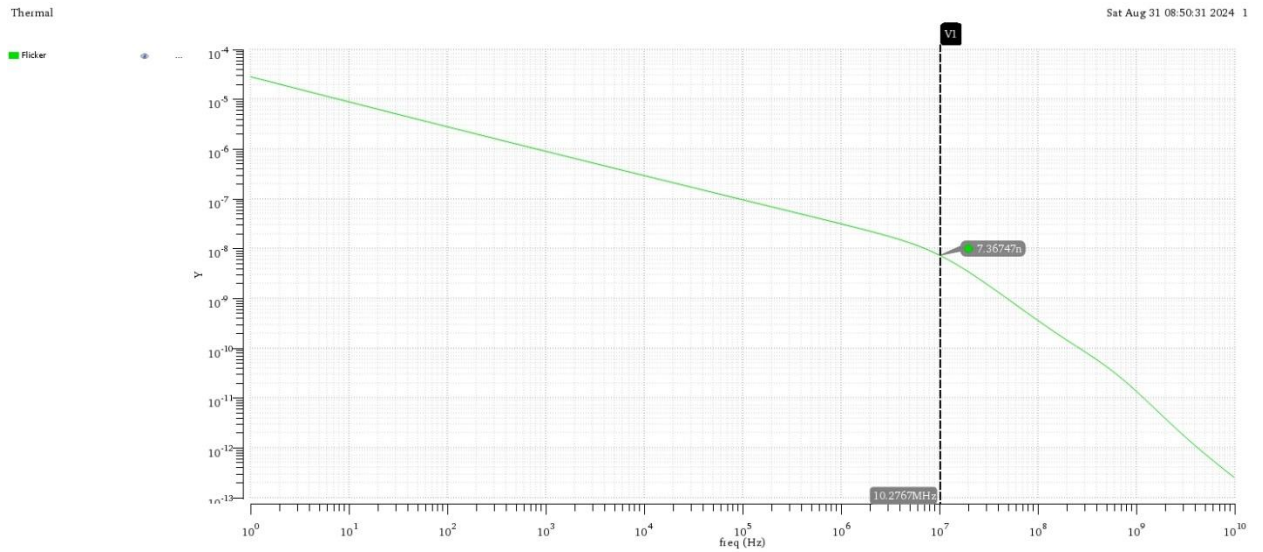

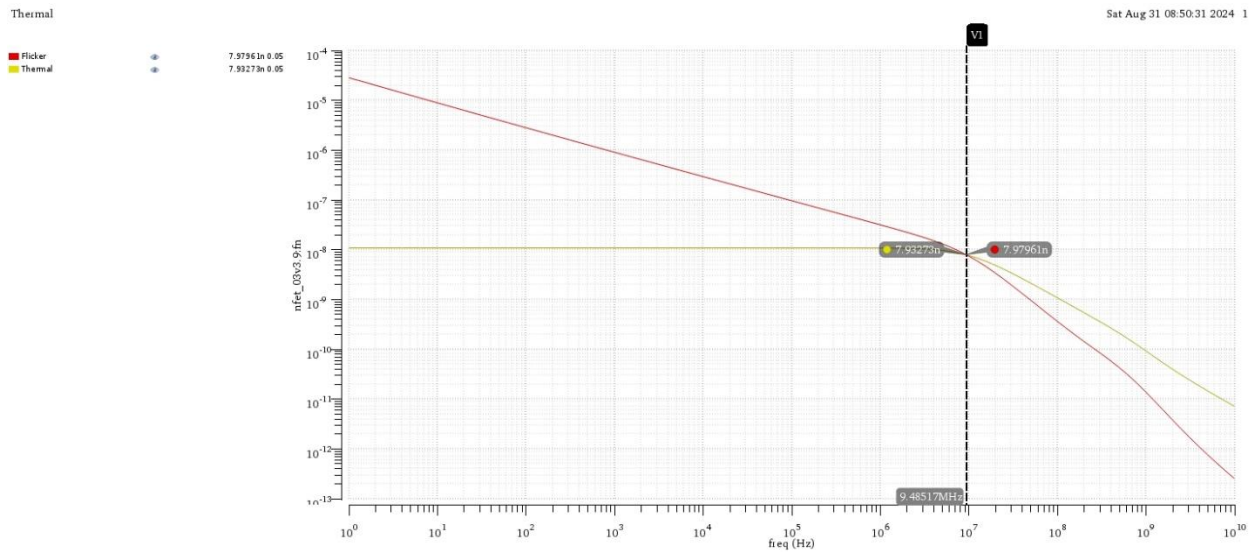3. Plotting thermal and flicker noise overlaid to Estimate the Flicker noise corner as y-axis is log scale



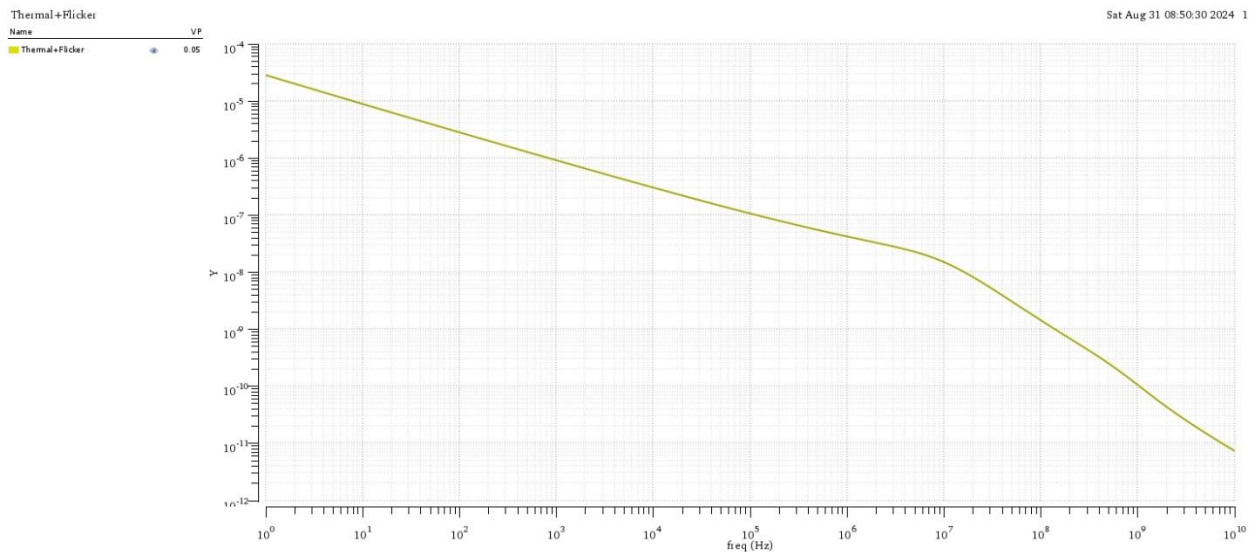1. Plotting total output noise (thermal + flicker) vs frequency as y-axis is log scale



- The RMS value of total output noise

| | | |
|------------------------|-----|--------|
| ITI_Su2024:5T_OTA_tb:1 | RMS | 127.7u |
|------------------------|-----|--------|

2. Calculate rms output noise (calculate the rms noise due to thermal noise only)

| Device | Param | Noise Contribution | % Of Total |
|----------|-------|--------------------|------------|
| I3.M1.m0 | fn | 6.04757e-09 | 37.09 |
| I3.M0.m0 | fn | 5.95408e-09 | 36.51 |
| I3.M2.m0 | fn | 1.20474e-09 | 7.39 |
| I3.M3.m0 | fn | 1.1901e-09 | 7.30 |
| I3.M0.m0 | id | 5.34127e-10 | 3.28 |
| I3.M1.m0 | id | 5.33016e-10 | 3.27 |
| I3.M3.m0 | id | 4.24969e-10 | 2.61 |
| I3.M2.m0 | id | 3.76821e-10 | 2.31 |
| I3.M5.m0 | fn | 1.94387e-11 | 0.12 |
| I3.M5.m0 | id | 1.24409e-11 | 0.08 |
| I3.M4.m0 | id | 4.99091e-12 | 0.03 |
| I3.M4.m0 | fn | 4.73686e-12 | 0.03 |

Integrated Noise Summary (in V²) Sorted By Noise Contributors
 Total Summarized Noise = 1.6307e-08
 Total Input Referred Noise = 4.4791e-06


- By take the root square of the sum of id the $V_{nrms} = 43.43\mu V$
- By hand analysis

$$V_{nrms} = \sqrt{V_n^2 * BW * \frac{\pi}{2}} = \sqrt{10.76 \frac{nV}{\sqrt{Hz}} * 10.19MHz * \frac{\pi}{2}} = 43.049\mu V$$

| | Simulation | Analysis |
|--------------------|---------------|----------------|
| Thermal V_{nrms} | 43.43 μV | 43.049 μV |


PART 4: 5T OTA Transient Noise Analysis

1. Plotting input and output overlaid

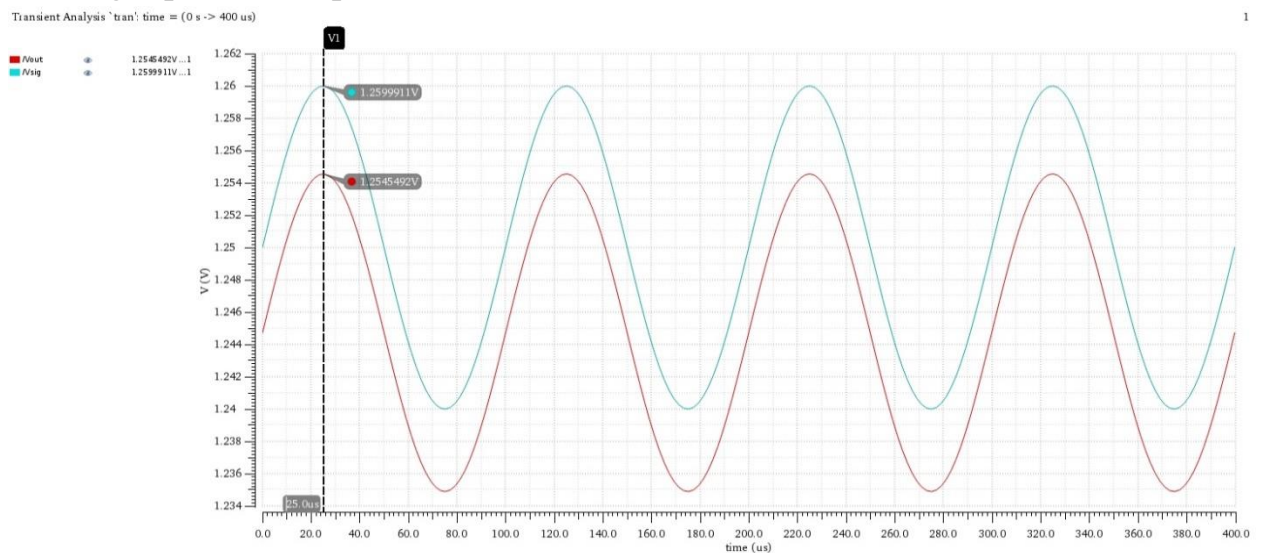


- There is V_{err} between the input and output as the amplifier has a finite gain


2. Plotting the “noisy” output waveform

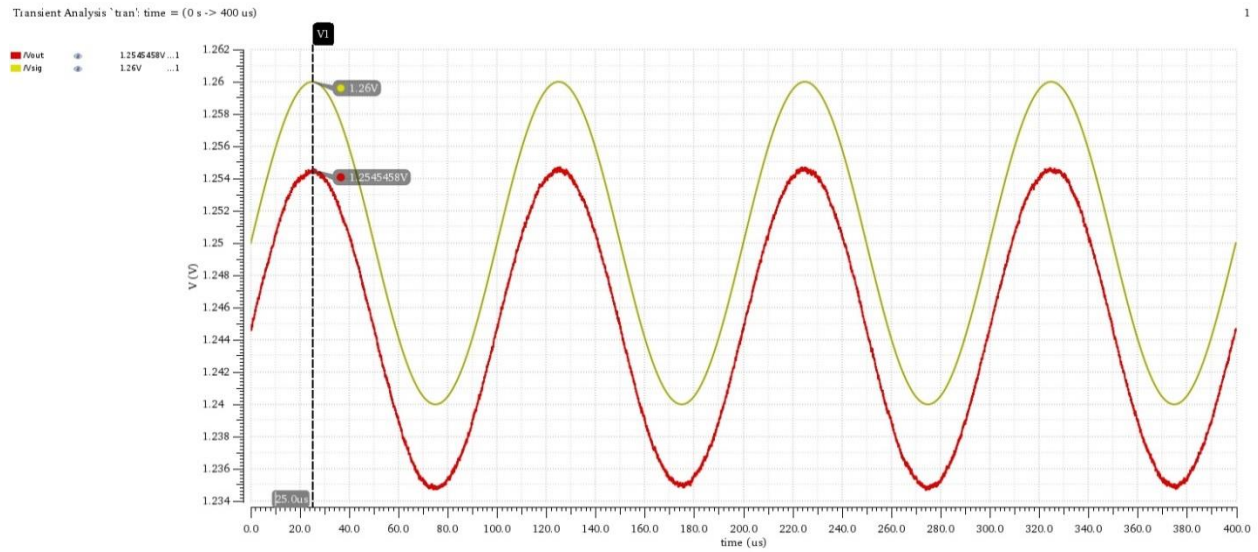

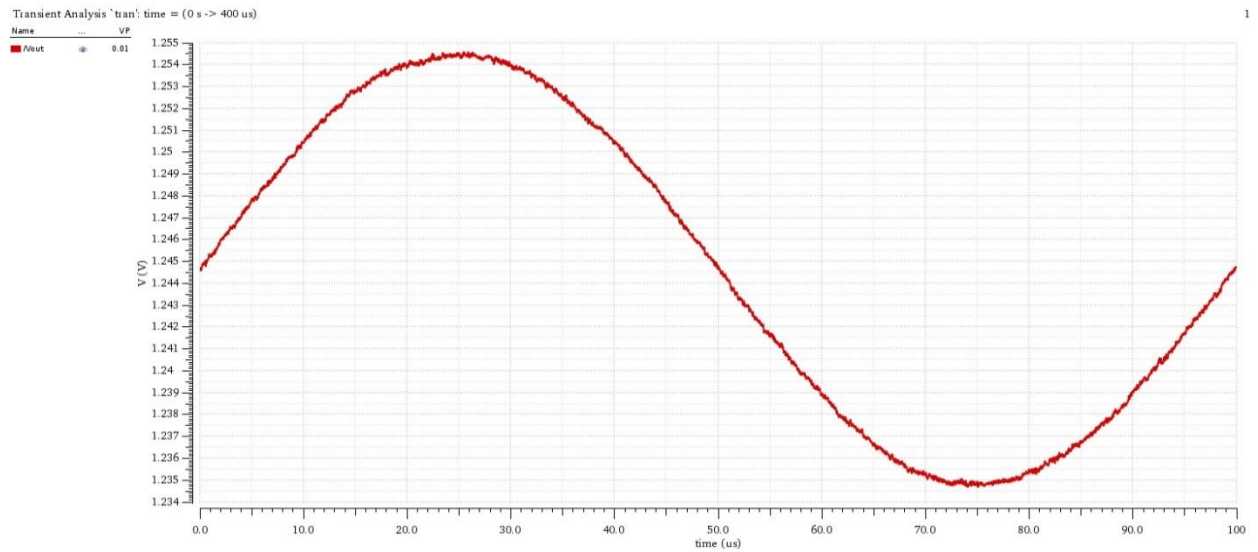
- One cycle of output waveform to highlight the noise



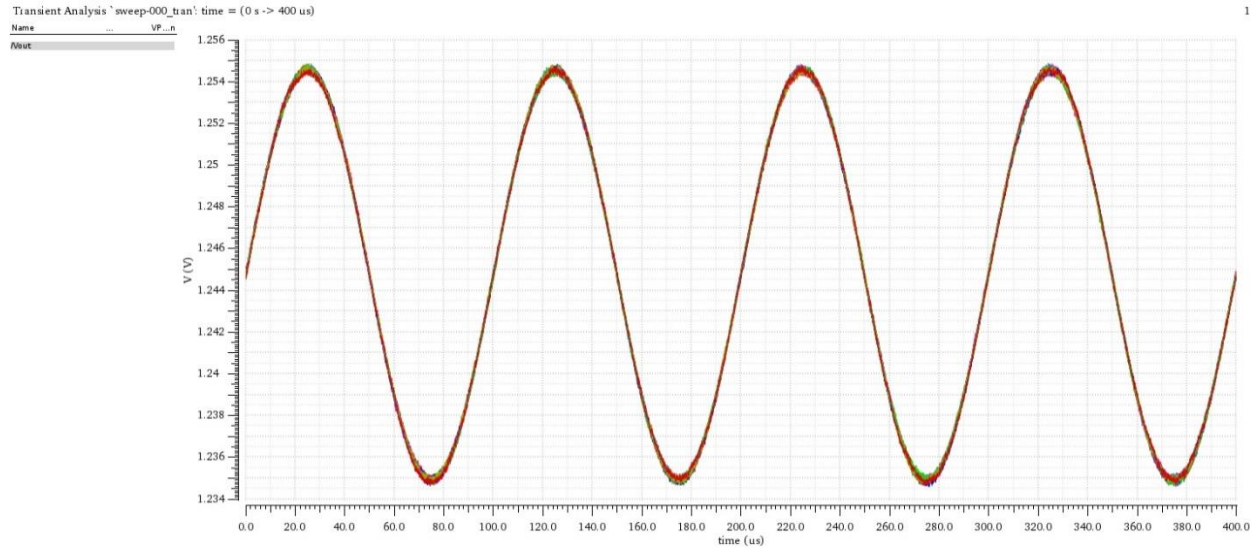3. plotting the output waveform after 20 simulation runs



4. Reporting the rms noise vs iteration.

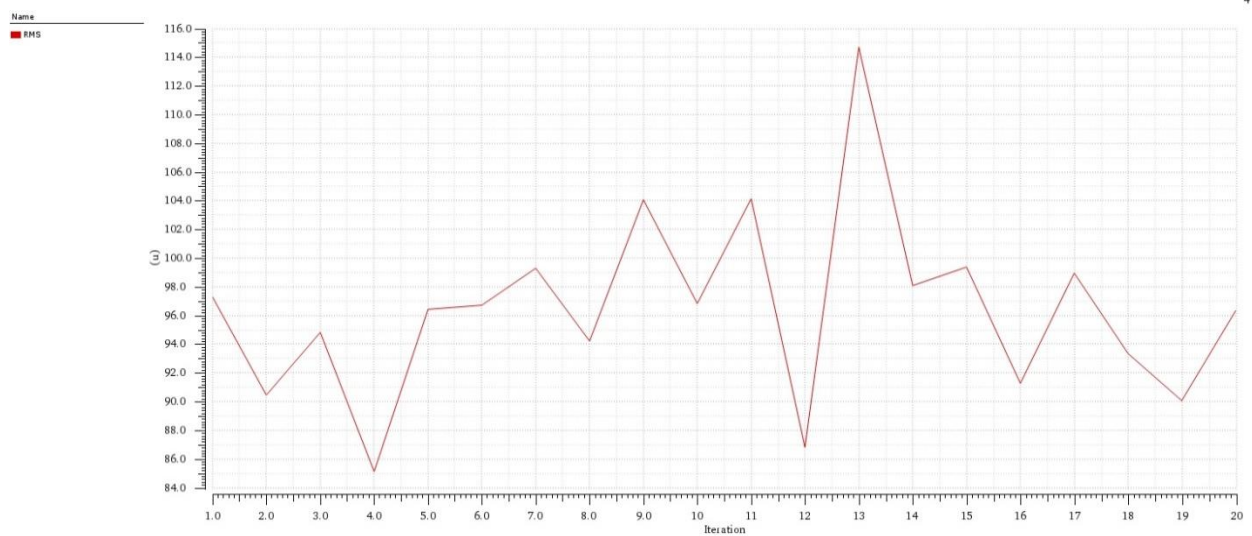

- The average value of the total noise

| VP | average...0.01)) |
|------------|------------------|
| 1 10.00E-3 | 96.42E-6 |

| | Part4 | Part3 |
|------------------|--------------|-------------------------------|
| Total V_{nrms} | 96.5 μV | $\sqrt{16.3nV} = 127.6 \mu V$ |