

ITI CMOS Analog IC Design 2024
Lab 02
Common Source Amplifier


PART 1: Sizing Chart

1. The specs we want to achieve for common source amplifier.

spec	Value
DC gain	-8
Supply	1.8 V
Current consumption	100 μ A


2. we will assume that $L=2\text{ }\mu\text{m}$ for get high r_o and avoid short channel effect
3. $|A_v| \approx gm * R_D = 2I_D * R_D / V_{ov} = 2V_{RD} / V_{ov}$
 - As $V_{ov} \neq 2I_D / gm$ in real MOSFET so we define $V^* = 2I_D / gm$
4. We make $V_{RD} = V_{DD} / 2$ to get the high swing so $V_{RD} = 1.8 / 2 = .9\text{ V}$
 $I_D * R_D = .9\text{ V}$ and $I_D = 100\text{ }\mu\text{A}$ then $R_D = 9\text{ K}\Omega$
5. then $2 V_{RD} / V_Q^* = 8$ then $V_Q^* = 225\text{mV}$
6. We use $W=10\text{ }\mu\text{m}$
7. As $V_{th} \approx 670\text{ mV}$, so $V_{th} + .4 \approx 1.1\text{V}$, so we sweep V_{GS} from 0mV to 1.1V

8. Plot V_{ov} and V^* Vs V_{GS}

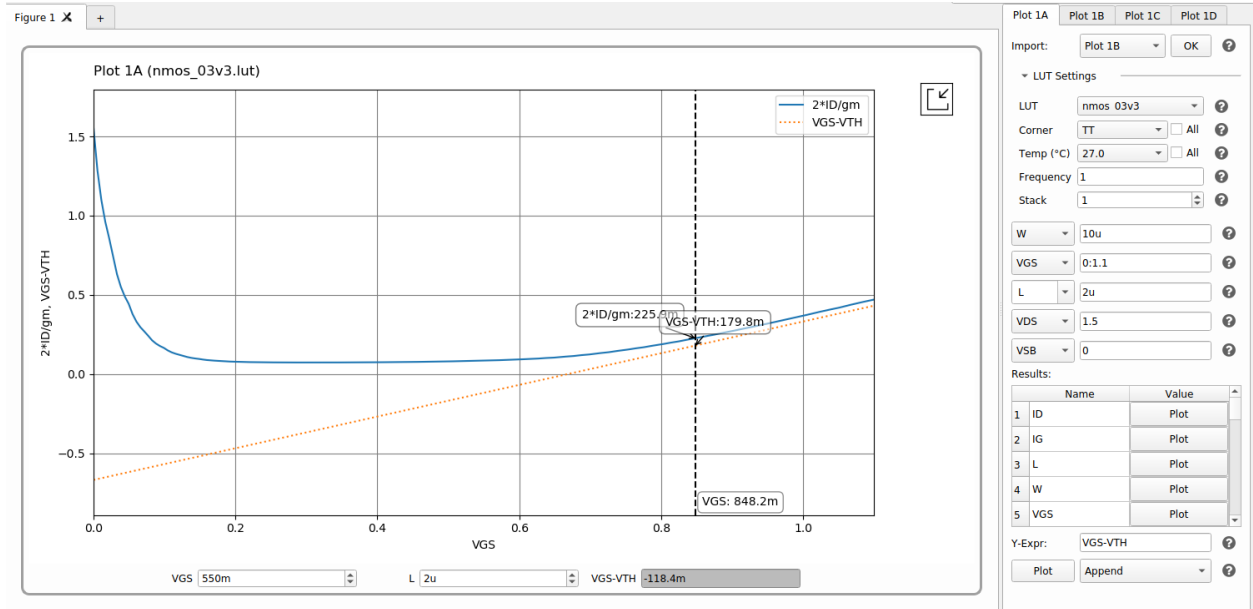

9. As we see that at $V_Q^* = 225.9 mV$ that $V_{ovQ} = 179.8 mV$ and $V_{GSQ} = 848.2 mV$

10. Plot gm and I_D and gds

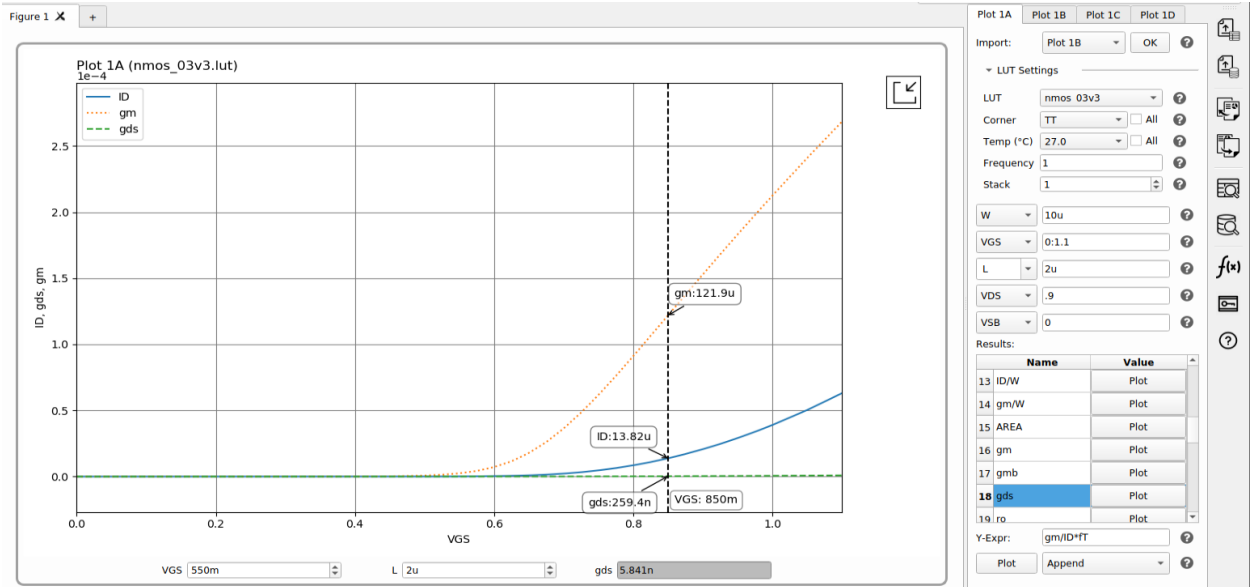

11.

@ $W = 10 \mu m$ and $V_{GS} = 850 mV$ and $L = 2 \mu m$		
I_{DX}	g_{mx}	g_{dsx}
$13.82 \mu A$	$121.9 \mu S$	$259.4 nS$

12. to get $I_D = 100 \mu A$ we need $W = 72.35 \mu m$

@ $W=72.35 \mu\text{m}$ and $V_{GS} = 850 \text{ mV}$ and $L=2 \mu\text{m}$		
I_D	g_m	g_{ds}
$100 \mu\text{A}$	$881.95 \mu\text{S}$	1876.76 nS


13. then we have $r_o = 1/g_{ds} = 532.83 \text{ k}\Omega$

- so, $A_v = -g_m R_D || r_o = -881.95 \times 10^{-6} \times (532.83 \text{ k}\Omega || 9 \text{ k}\Omega) = -7.81$
so we meet the specs mentioned above

PART 2: CS Amplifier

1. OP and AC Analysis

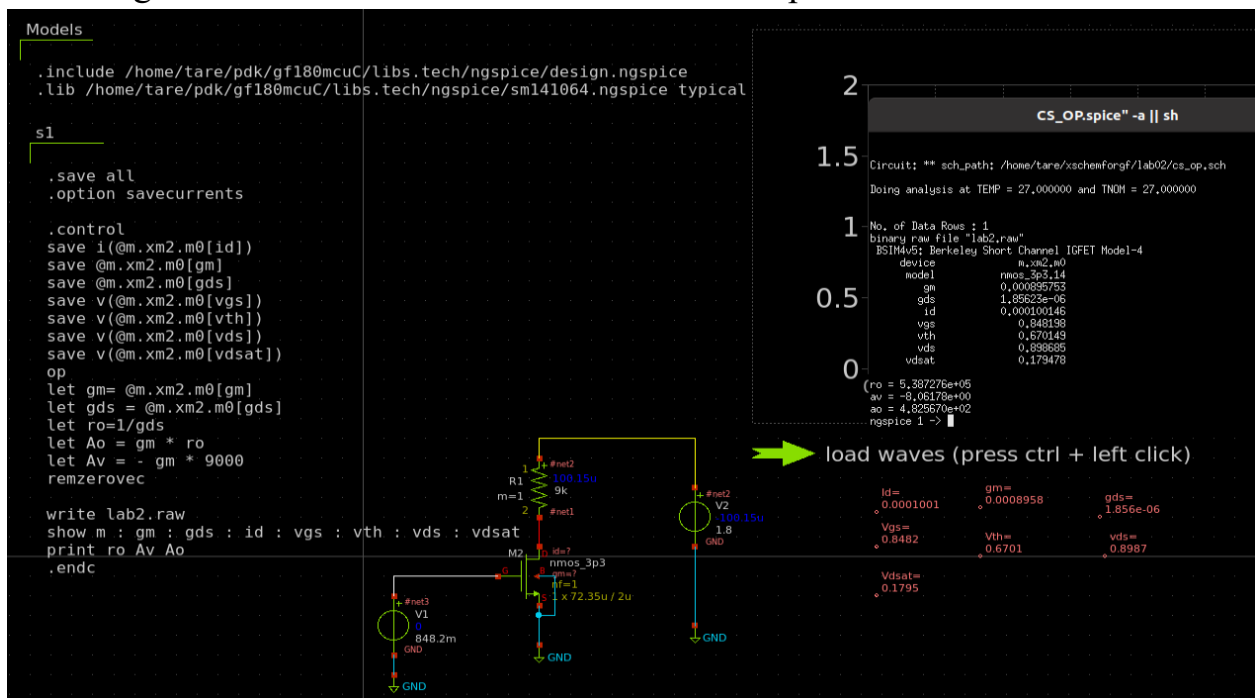1. Creating a testbench for the resistive loaded CS amplifier




2. Simulating the DC OP.

parameter	I_D	g_m	g_{ds}
Simulation	$100.1 \mu\text{A}$	$895.8 \mu\text{S}$	$1.856 \mu\text{S}$
Sizing Chart	$100 \mu\text{A}$	$881.95 \mu\text{S}$	1876.76 nS

- The two value are approximately equal.
3. $r_o = 538.8 \text{ k}\Omega$, so $r_o/R_D = 59.87$ then $r_o \gg R_D$ so $r_o || R_D \approx R_D$
 - we can ignore r_o in our case
 - $r_o \propto L$ so as L decrease r_o decrease and this will affect the gain of the circuit.
 4. intrinsic gain equal $g_m * r_o = g_m / g_{ds} = 895.8 \mu\text{S} / 1.856 \mu\text{S} = 482.65$
 5. the gain of this circuit equal $-\frac{g_m}{1+(g_m+g_{mb})R_s} * r_o || R_D$

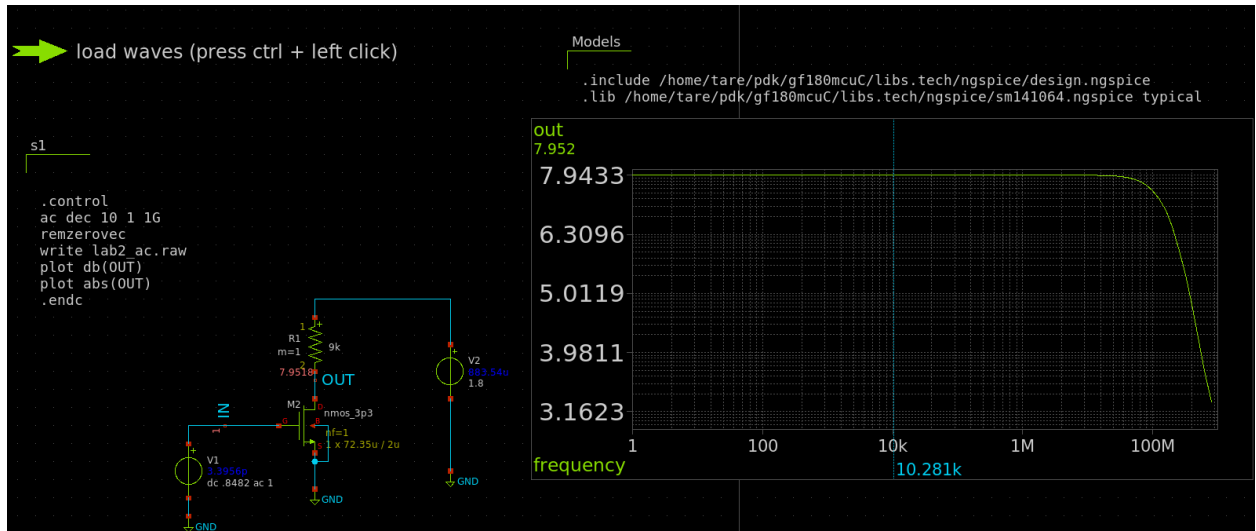
- there are no body effect and no R_s then gain equal $-g_m \cdot r_o \parallel R_D$
 $= -895.8 \mu S \cdot (538.8 k\Omega \parallel 9 k\Omega) = -7.93$
- we notice that $g_m \cdot r_o \gg g_m \cdot r_o \parallel R_D$



6. when applying ac voltage = 1 V we get output voltage = 7.952V this mean we have dc gain equal 7.952


2. Gain Non-Linearity

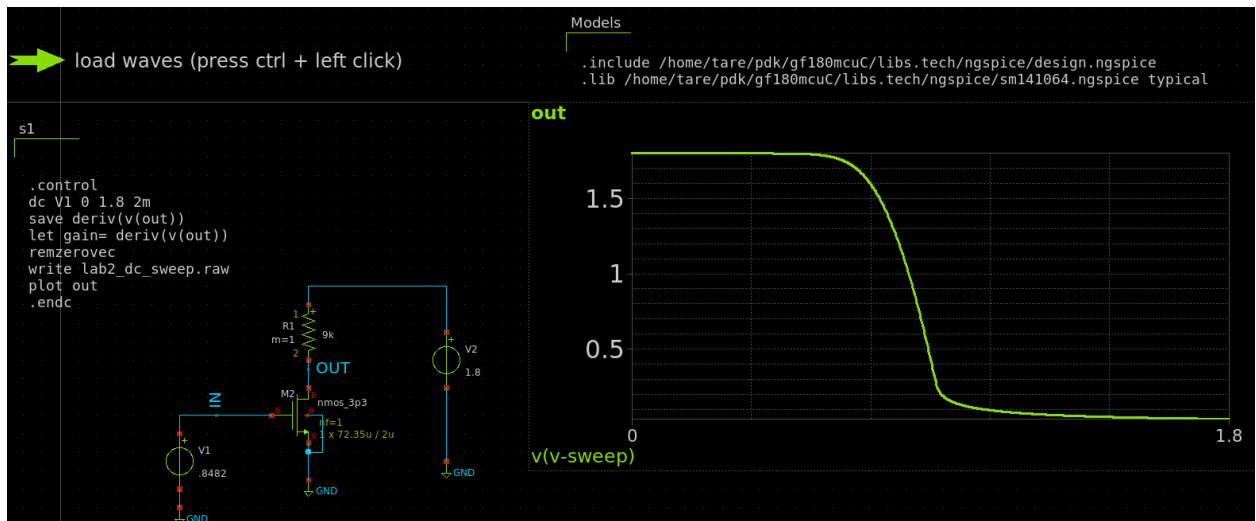1. Performing a DC sweep for the input voltage from 0 to V_{DD} with 2mV step.
2. V_{OUT} vs V_{IN}




- We see that the relation is not linear there are three region

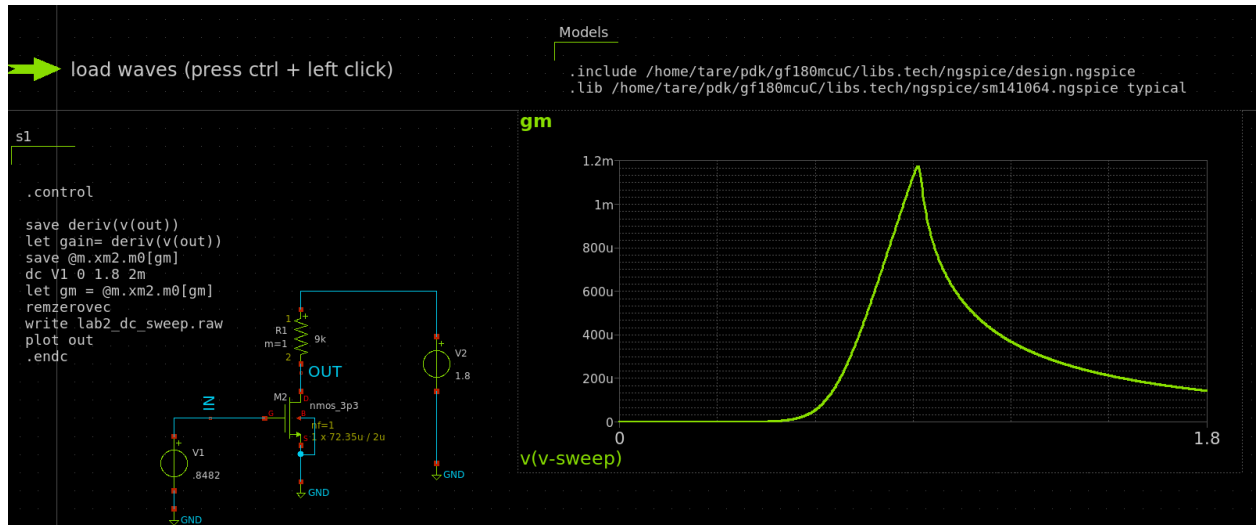
- first one the transistor is still off so V_{out} is constant and equal $V_{DD} = 1.8V$



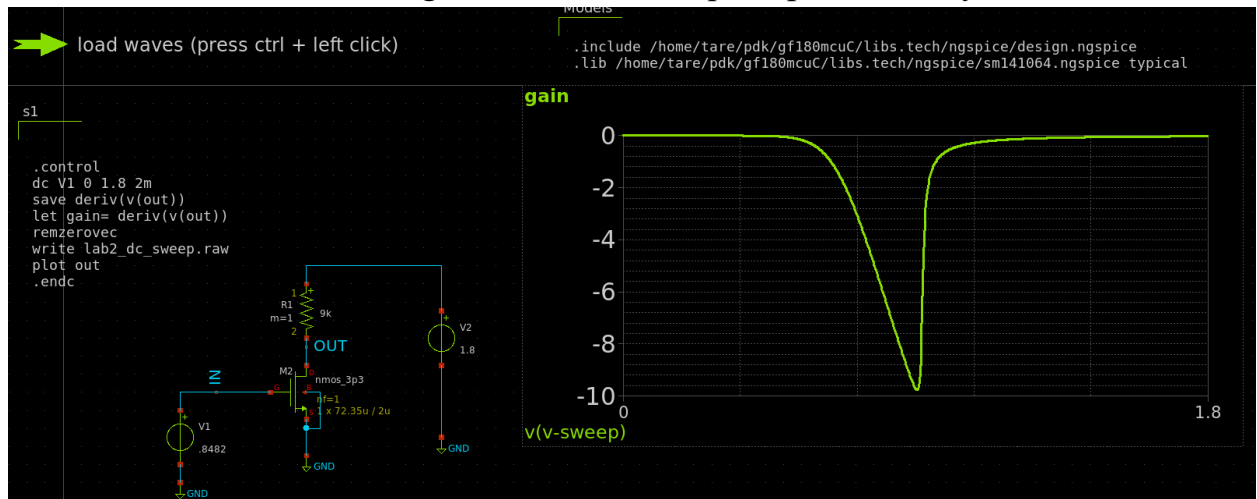
- second one is the saturation region and the MOSFET amplify the signal and it is not linear because gm changing with changing of the input voltage.
- third one is the the triode region and the V_{out} equal approximately 0



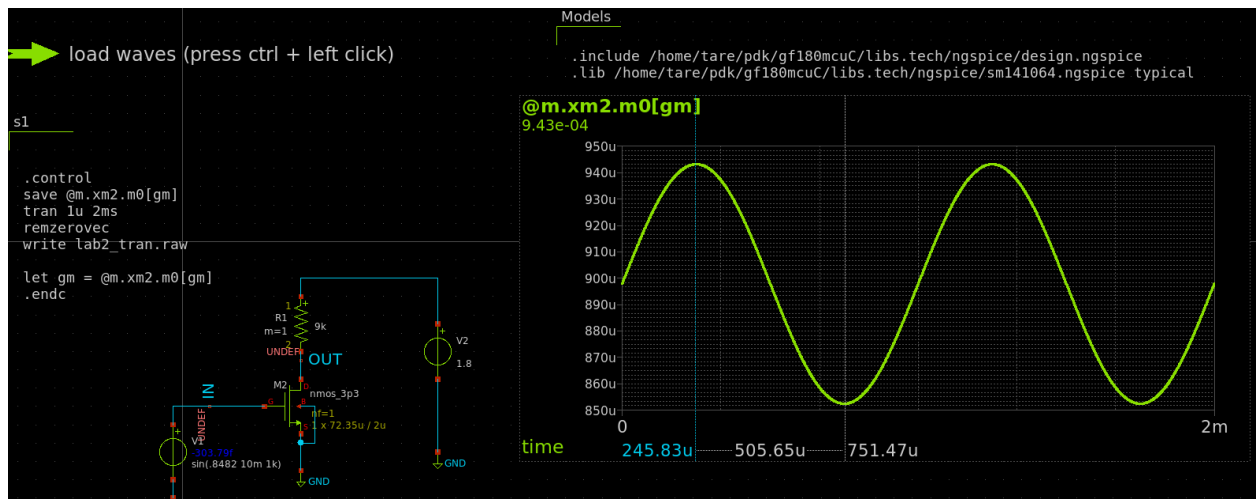3. gain isn't linear because it depend on gm and $gm \propto V_{in}$ as W/L is constant.
From the gm Vs V_{in} grap $\Delta gm = 943 - 851 = 92 \mu S$



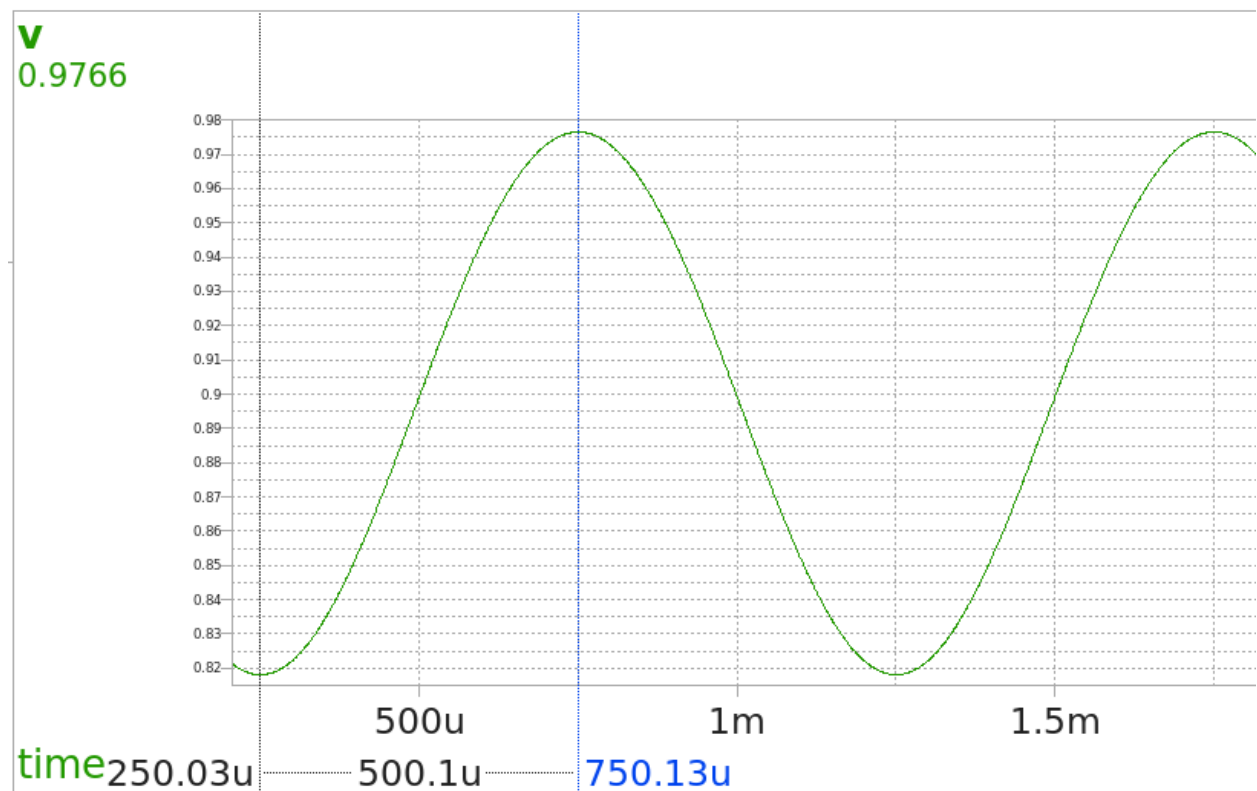4. the peak to peak $V_{out} = 976.6 - 818.1 = 158.5\text{mV}$ and peak to peak $V_{in} = 20\text{mV}$
so dc gain $= 158.5/20 = 7.925$



5. g_m vary with the input signal as $g_m \propto V_{in}$ that mean the gain isn't linear but it varying slightly with the input voltage.
6. The amplifier isn't typically linear but it vary with the input signal.

- From V_{out} Vs time figure above we can think it idle sine wave but its down peak bigger than the up peak because down peak from the output come from the up peak of the input and up peak has bigger g_m and bigger amplification
- Biasing V_{ds} voltage $= 1.8 - 100.1 \mu A * 9 k\Omega = 899.1 \text{ mV}$
- Down peak $= 899.1 - 818.1 = 81 \text{ mV}$
- Up peak $= 976.6 - 889.1 = 77.5 \text{ mV}$